
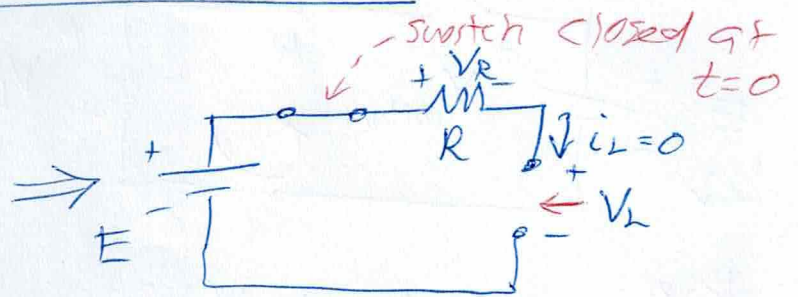




At  $t=0$  (initial conditions)

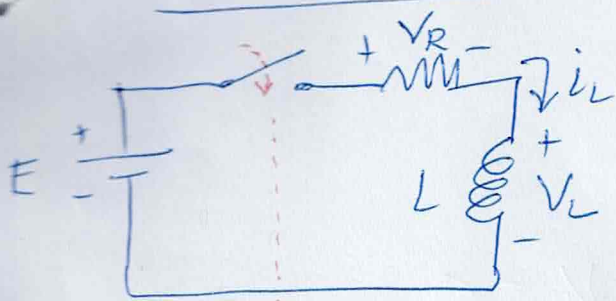




Just before switch is closed  $\rightarrow$  No current  $i_L$  flows into inductor, so inductor  $L$  acts as an open circuit

$$V_L = E$$

At  $t = \infty$  (steady state)

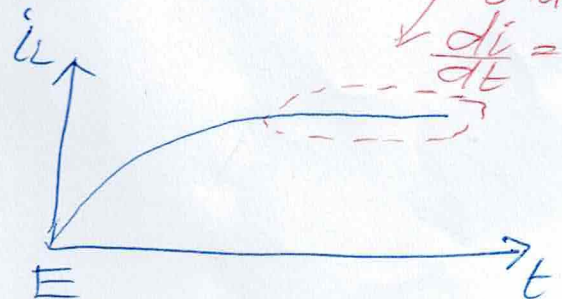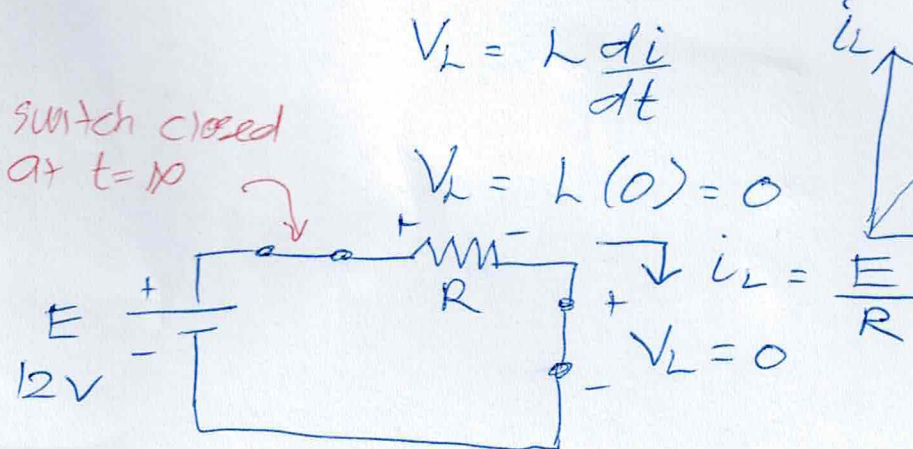


At  $t = \infty$ , switch is opened

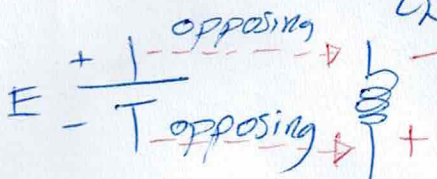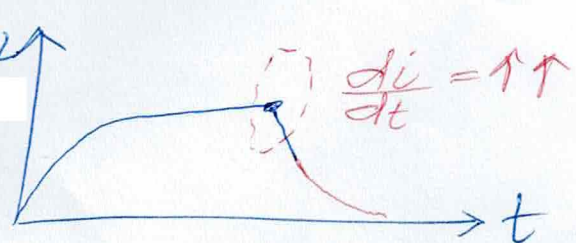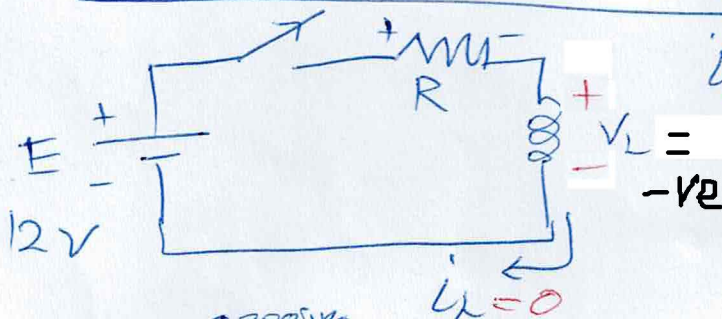

Faraday's Law  $\Rightarrow$  induced  $V_L$  opposing sudden change of  $i_L$

$$V_L = L \left( \frac{di_L}{dt} \right)$$
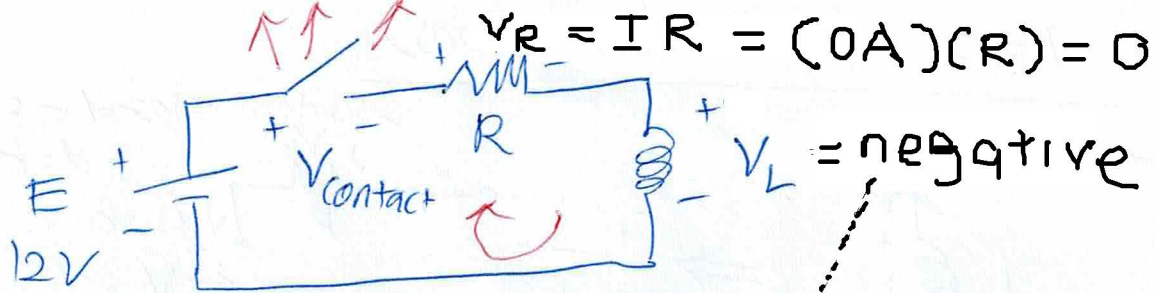
$$V_L \uparrow \uparrow \text{ because } \frac{di_L}{dt} \uparrow \uparrow$$



KVL

$$-12 + V_{\text{contact}} + (-V_L) = 0$$

$$V_{\text{contact}} = V_L + 12$$

↑↑

↑↑

spark plug

ignition coil

example


$$V_L = L \left( \frac{di}{dt} \right)$$

1A  $\rightarrow$  0A  
in  $10^{-6}$  seconds


$$\text{if } \frac{di}{dt} = \frac{1}{10^{-6}}$$
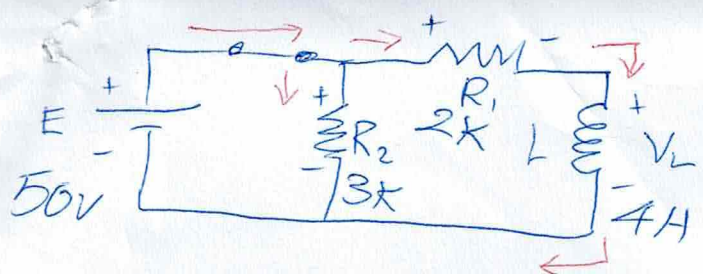
$$V_L \approx 10\text{MV} (10 \times 10^6 \text{V})$$





Thevenin

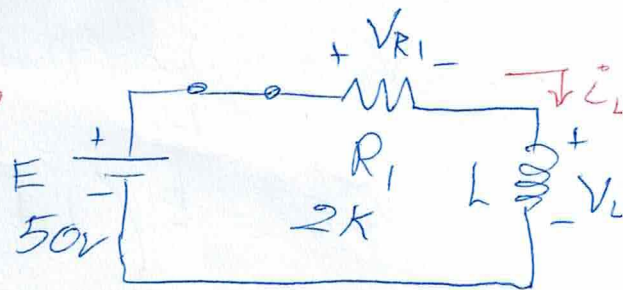

at  $t = \infty$  (steady state) (switch is closed)

$$\tau_1 = \frac{L}{R_1} = \frac{4H}{2k} = 2ms$$

$$i_L = \frac{E}{R_1} (1 - e^{-\frac{t}{2ms}}) = \frac{50V}{2k} (1 - e^{-\frac{t}{2ms}})$$


$$i_L = 25mA (1 - e^{-\frac{t}{2ms}})$$

$$V_L = E (e^{-\frac{t}{2ms}}) = 50V e^{-\frac{t}{2ms}}$$

$$V_{R1} = i_L R_1 = (2k)(25mA)(1 - e^{-\frac{t}{2ms}})$$

$$V_{R1} = (50V)(1 - e^{-\frac{t}{2ms}})$$

Switch is opened

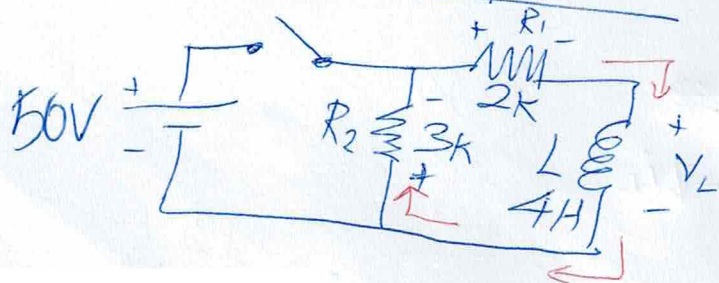

$$\tau_2 = \frac{L}{R_1 + R_2} = \frac{4H}{2k + 3k} = 0.8ms$$

(KVL)  $V_{R2} + V_{R1} + V_L = 0$

$$V_L = -(V_{R1} + V_{R2})$$

$$V_L = -i_L (R_1 + R_2)$$

A change in current induces voltage in L

Just before switch is opened

is opened

(at  $t = \infty$ )

Steady state)

$$i_L = \frac{E}{R_1}$$

$$i_L = 25mA$$

(negative  $V_L$ )

$$i_L = 25mA (1 - e^{-\frac{t}{2ms}})$$

$$V_L = -\frac{E}{R_1} (R_1 + R_2)$$

$$V_L = -E \left( 1 + \frac{R_2}{R_1} \right)$$

$$V_L = -50 \left( 1 + \frac{3k}{2k} \right) = -125V$$

Faraday's Law  
Induced voltage opposing  
sudden change of  $i_L$   
..(negative)

$$I_L = 25mA$$

(KVL)



$$V_{R2} + V_{R1} + V_L = 0$$

$$V_{R1} = (I_L) R_1 = (25mA)(2k) = 50V$$

$$V_{L1} = -125V$$

$$V_{R2} + 50V - 125V = 0$$

$$V_{R2} = 75V$$

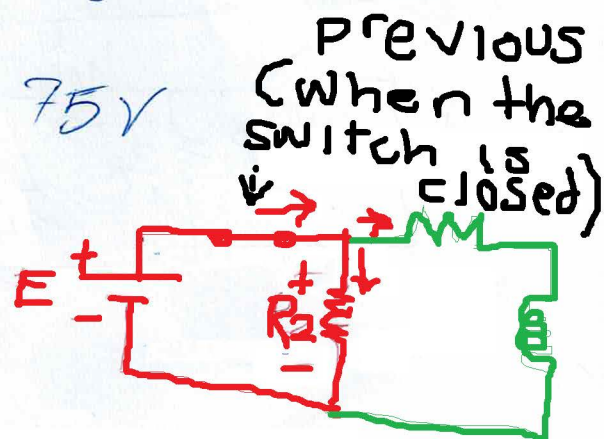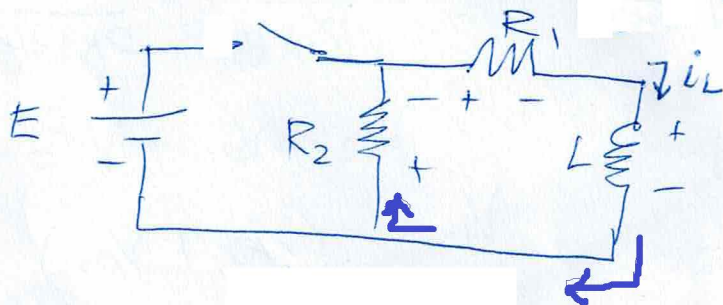


$$\text{Hence } V_{R2} = -75V$$

because current  $\uparrow$  is opposite  
to previous  
current  $\downarrow$



When switch is opened

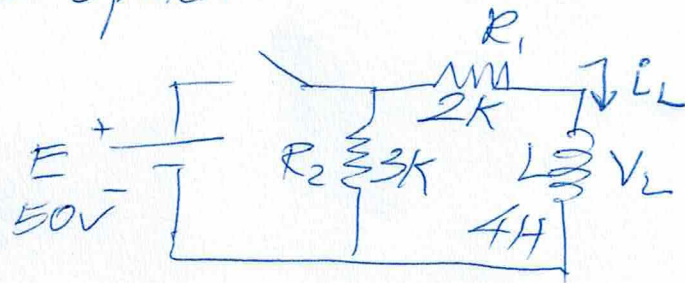


$$\tau_2 = \frac{L}{R_1 + R_2} = \frac{4H}{2K + 3K} = 0.8ms$$


$$V_L = -125V \left( e^{-\frac{t}{0.8ms}} \right)$$

$$I_L = 25mA \left( e^{-\frac{t}{0.8ms}} \right)$$

Switch closed  
( $t = \infty$ )

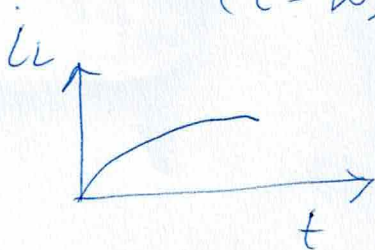

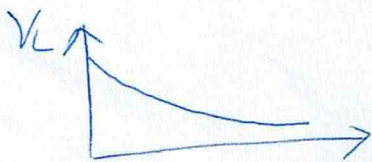
$$i_L = \frac{E}{R_1} \left( 1 - e^{-\frac{t}{\tau_1}} \right)$$




$$V_L = E \left( e^{-\frac{t}{\tau_1}} \right)$$

switch opened

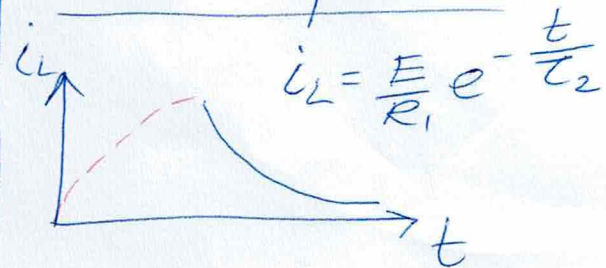
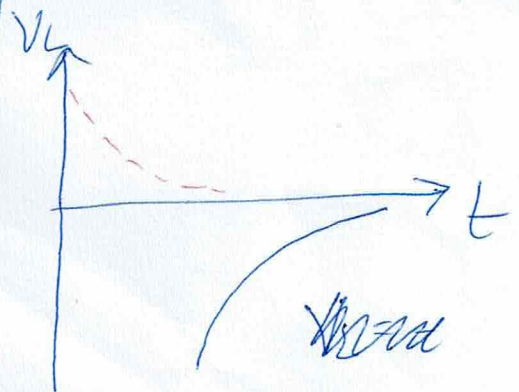
$$i_L = \frac{E}{R_1} e^{-\frac{t}{\tau_2}}$$



$$V_L = -E \left( 1 + \frac{R_2}{R_1} \right) e^{-\frac{t}{\tau_2}}$$