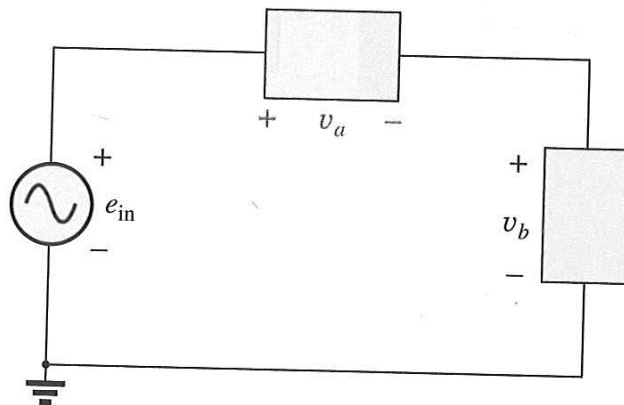


ENGG104 Tutorial 10 Class Questions

Team Name: _____

Question 1 - [past exam question]



$$e_{in} = 60 \sin(377t + 45^\circ)$$

$$v_b = 20 \sin(377t - 45^\circ)$$

In the above circuit, e_{in} and v_b are given, determine the expression for v_a .

(Using peak values)


$$e_{in} = v_a + v_b \Rightarrow v_a = e_{in} - v_b$$

$$= 60 \text{ V } \angle 45^\circ - 20 \text{ V } \angle -45^\circ$$

$$= 63.25 \text{ V } \angle 63.43^\circ$$

and $e_{in} = 63.25 \sin(377t + 63.43^\circ)$

QUESTION 2 - [past exam question]

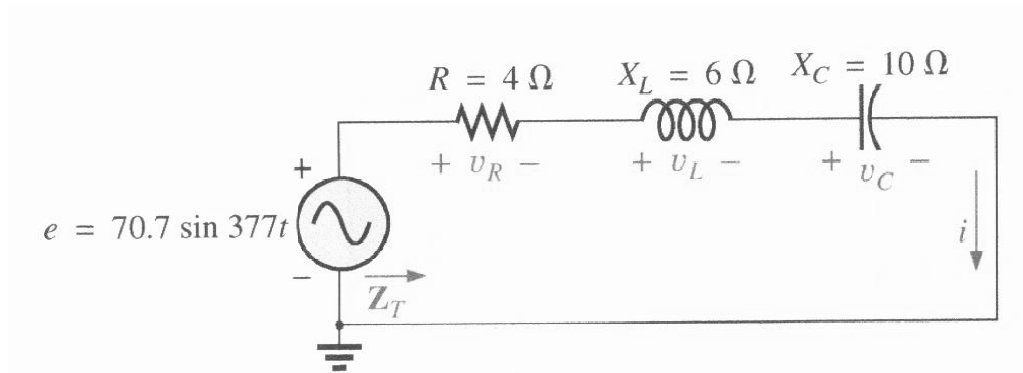

For the circuit above, find Z_T , X_L , X_C , I , V_R , V_L , V_C , Power delivered to the 4 Ohms resistor, and the power factor F_p

a. $Z_T = 4 \Omega + j6 \Omega - j10 \Omega = 4 \Omega - j4 \Omega = 5.66 \Omega \angle -45^\circ$

c. $X_L = \omega L \Rightarrow L = \frac{X_L}{\omega} = \frac{6 \Omega}{377 \text{ rad/s}} = 16 \text{ mH}$

$X_C = \frac{1}{\omega C} \Rightarrow C = \frac{1}{\omega X_C} = \frac{1}{(377 \text{ rad/s})(10 \Omega)} = 265 \mu\text{F}$

d. $I = \frac{E}{Z_T} = \frac{50 \text{ V} \angle 0^\circ}{5.66 \Omega \angle -45^\circ} = 8.83 \text{ A} \angle 45^\circ$

$V_R = (I \angle \theta)(R \angle 0^\circ) = (8.83 \text{ A} \angle 45^\circ)(4 \Omega \angle 0^\circ) = 35.32 \text{ V} \angle 45^\circ$

$V_L = (I \angle \theta)(X_L \angle 90^\circ) = (8.83 \text{ A} \angle 45^\circ)(6 \Omega \angle 90^\circ) = 52.98 \text{ V} \angle 135^\circ$

$V_C = (I \angle \theta)(X_C \angle -90^\circ) = (8.83 \text{ A} \angle 45^\circ)(10 \Omega \angle -90^\circ) = 88.30 \text{ V} \angle -45^\circ$

f. $E = V_R + V_L + V_C$


$50 \text{ V} \angle 0^\circ = 35.32 \text{ V} \angle 45^\circ + 52.98 \text{ V} \angle 135^\circ + 88.30 \text{ V} \angle -45^\circ$

$50 \text{ V} \angle 0^\circ = 49.95 \text{ V} \angle 0^\circ \cong 50 \text{ V} \angle 0^\circ$

g. $P = I^2 R = (8.83 \text{ A})^2 4 \Omega = 311.88 \text{ W}$


h. $F_p = \cos \theta_T = \frac{R}{Z_T} = 4 \Omega / 5.66 \Omega = 0.707 \text{ leading}$

QUESTION 3 - [past exam question]

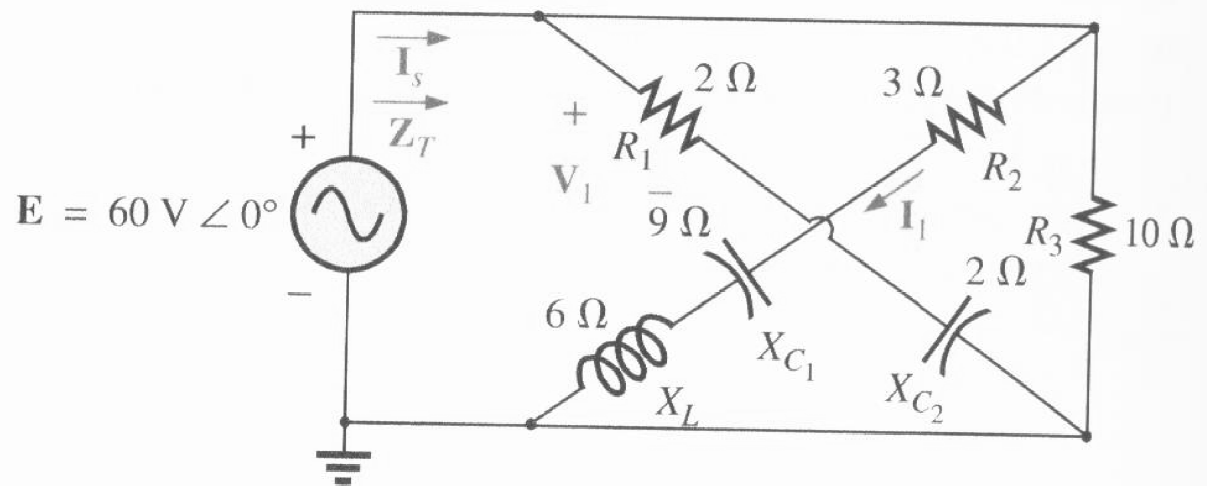

For the circuit above, find Z_T , V_1 , I_1 , and I_s

a.

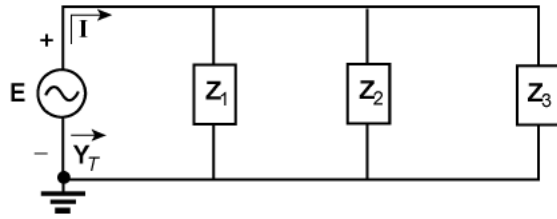

$$Z_1 = 2 \, \Omega - j2 \, \Omega = 2.828 \, \Omega \angle -45^\circ$$

$$Z_2 = 3 \, \Omega - j9 \, \Omega + j6 \, \Omega$$

$$= 3 \, \Omega - j3 \, \Omega = 4.243 \, \Omega \angle -45^\circ$$

$$Z_3 = 10 \, \Omega \angle 0^\circ$$

$$Y_T = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} = \frac{1}{2.828 \, \Omega \angle -45^\circ} + \frac{1}{4.243 \, \Omega \angle -45^\circ} + \frac{1}{10 \, \Omega \angle 0^\circ}$$

$$= 0.354 \, \text{S} \angle 45^\circ + 0.236 \, \text{S} \angle 45^\circ + 0.1 \, \text{S} \angle 0^\circ = 0.59 \, \text{S} \angle 45^\circ + 0.1 \, \text{S} \angle 0^\circ$$

$$= 0.417 \, \text{S} + j0.417 \, \text{S} + 0.1 \, \text{S}$$

$$Y_T = 0.517 \, \text{S} + j0.417 \, \text{S} = \mathbf{0.66 \, \text{S} \angle 38.89^\circ}$$

$$Z_T = \frac{1}{Y_T} = \frac{1}{0.66 \, \text{S} \angle 38.89^\circ} = \mathbf{1.52 \, \Omega \angle -38.89^\circ}$$

b. $V_1 = \frac{(2 \, \Omega \angle 0^\circ)(60 \, \text{V} \angle 0^\circ)}{2 \, \Omega - j2 \, \Omega} = \frac{120 \, \text{V} \angle 0^\circ}{2.828 \angle -45^\circ} = \mathbf{42.43 \, \text{V} \angle 45^\circ}$

c. $I_1 = \frac{E}{Z'} = \frac{60 \, \text{V} \angle 0^\circ}{3 \, \Omega - j9 \, \Omega + j6 \, \Omega} = \frac{60 \, \text{V} \angle 0^\circ}{3 \, \Omega - j3 \, \Omega} = \frac{60 \, \text{V} \angle 0^\circ}{4.243 \angle -45^\circ}$
 $= \mathbf{14.14 \, \text{A} \angle 45^\circ}$

d. $I_s = \frac{E}{Z_T} = \frac{60 \, \text{V} \angle 0^\circ}{1.52 \, \Omega \angle -38.89^\circ} = \mathbf{39.47 \, \text{A} \angle 38.89^\circ}$