

# ENGG104 Tutorial 5 Class Questions

Team Name: \_\_\_\_\_

## Question 1 [typical exam question]

Using superposition, find the voltage  $V_2$  for the network in Fig. 9.123.



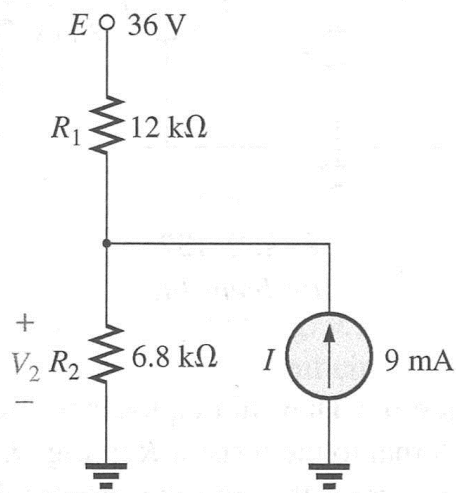
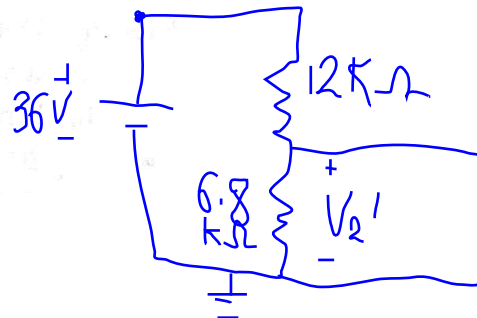


FIG. 9.123

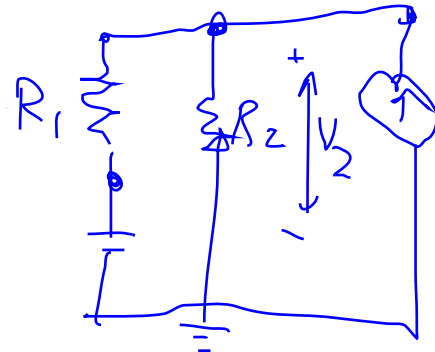
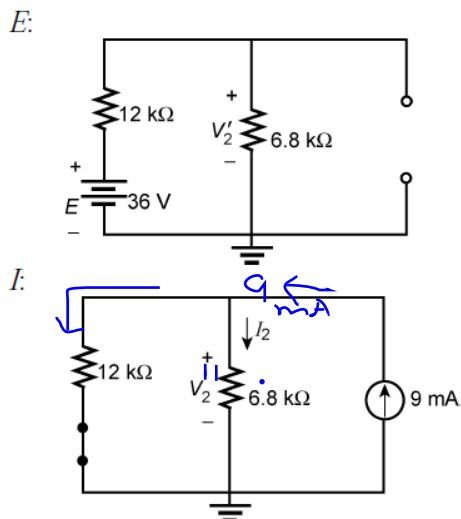
$$V_2' = \frac{6.8 \text{ k}\Omega (36 \text{ V})}{6.8 \text{ k}\Omega + 12 \text{ k}\Omega} = 13.02 \text{ V}$$



$$I_2 = \frac{12 \text{ k}\Omega (9 \text{ mA})}{12 \text{ k}\Omega + 6.8 \text{ k}\Omega} = 5.75 \text{ mA}$$

$$V_2'' = I_2 R_2 = (5.75 \text{ mA})(6.8 \text{ k}\Omega) = 39.10 \text{ V}$$

$$V_2 = V_2' + V_2'' = 13.02 \text{ V} + 39.10 \text{ V} = \mathbf{52.12 \text{ V}}$$

## Question 2

- Find the Thévenin equivalent circuit for the network external to the resistor  $R$  in Fig. 9.126.
- Find the current through  $R$  when  $R$  is  $2\ \Omega$ ,  $30\ \Omega$ , and  $100\ \Omega$ .



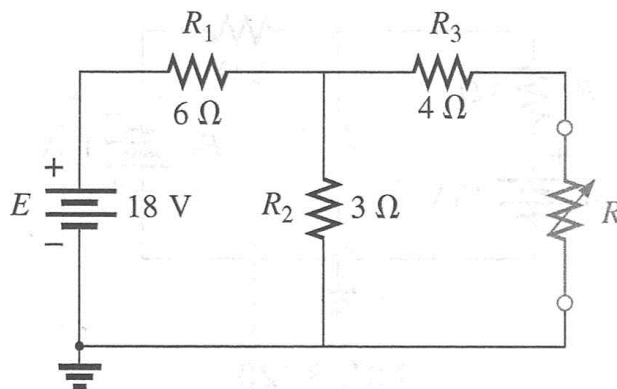



FIG. 9.126

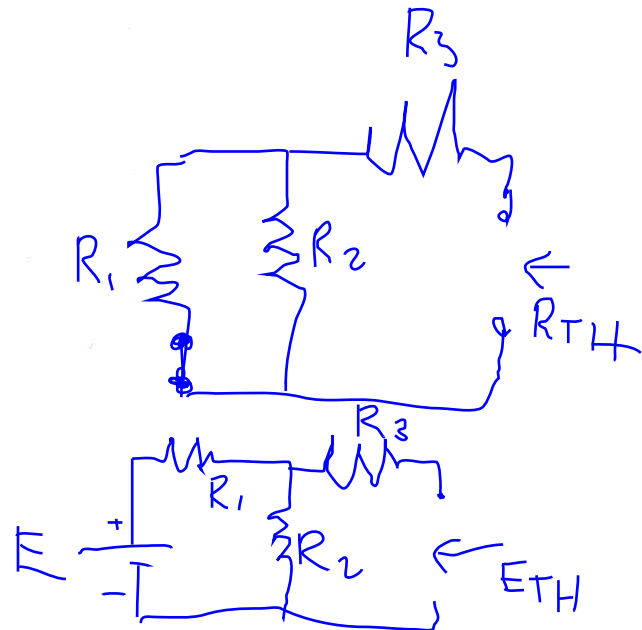
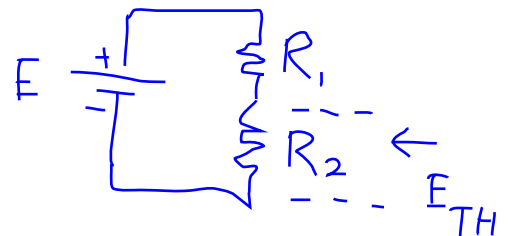
$$\begin{aligned} \text{a. } R_{Th} &= R_3 + (R_1 \parallel R_2) = 4\ \Omega + (6\ \Omega \parallel 3\ \Omega) = 4\ \Omega + 2\ \Omega = 6\ \Omega \\ E_{Th} &= \frac{R_2 E}{R_2 + R_1} = \frac{3\ \Omega (18\ \text{V})}{3\ \Omega + 6\ \Omega} = 6\ \text{V} \end{aligned}$$



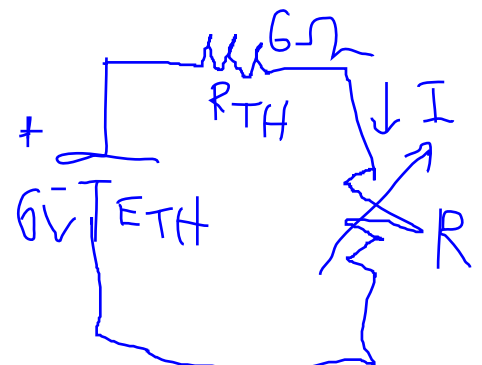
$$\begin{aligned} \text{b. } I_1 &= \frac{E_{Th}}{R_{Th} + R} = \frac{6\ \text{V}}{6\ \Omega + 2\ \Omega} = 0.75\ \text{A} \\ I_2 &= \frac{6\ \text{V}}{6\ \Omega + 30\ \Omega} = 166.67\ \text{mA} \\ I_3 &= \frac{6\ \text{V}}{6\ \Omega + 100\ \Omega} = 56.60\ \text{mA} \end{aligned}$$




**Question 3** [typical exam question]


- Find the Thévenin equivalent circuit for the network external to the resistor  $R$  for the network in Fig. 9.127.
- Find the power delivered to  $R$  when  $R$  is  $2\text{ k}\Omega$  and  $100\text{ k}\Omega$ .

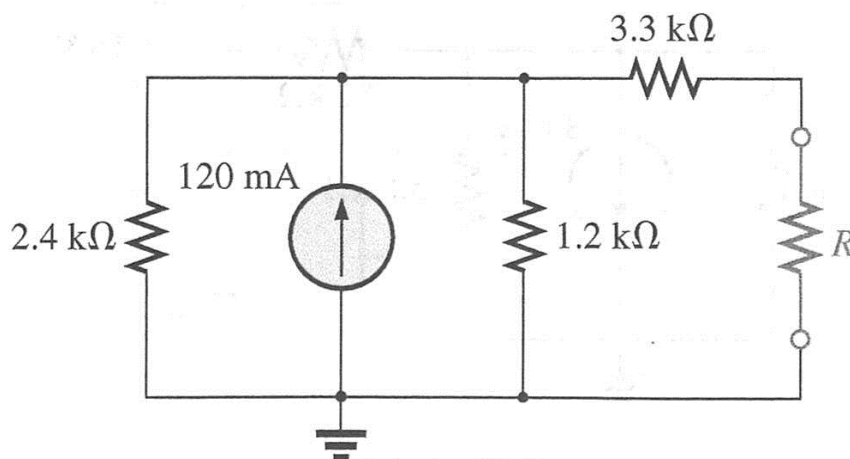

**FIG. 9.127**

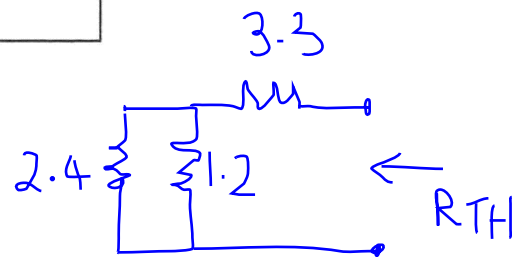


a.  $R_{Th}$ :

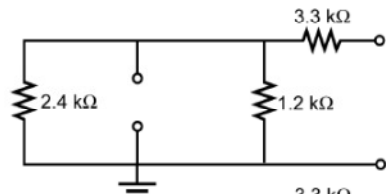


$$\begin{aligned} R_{Th} &= 3.3\text{ k}\Omega + (1.2\text{ k}\Omega \parallel 2.4\text{ k}\Omega) \\ &= 3.3\text{ k}\Omega + 0.8\text{ k}\Omega \\ &= 4.1\text{ k}\Omega \end{aligned}$$

← a


$E_{Th}$ :

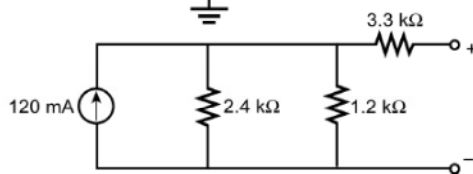
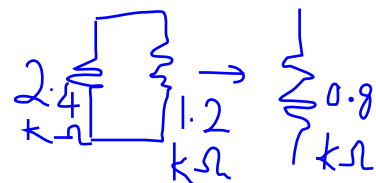
$$\begin{aligned} E_{Th} &= (120\text{ mA})(2.4\text{ k}\Omega \parallel 1.2\text{ k}\Omega) \\ &= 96\text{ V} \end{aligned}$$



b.

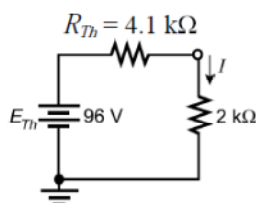

$$\begin{aligned} I &= \frac{96\text{ V}}{6.1\text{ k}\Omega} = 15.74\text{ mA} \\ P &= I^2 R = (15.74\text{ mA})^2 2\text{ k}\Omega = 0.495\text{ W} \\ R &= 100\text{ k}\Omega: \\ I &= \frac{96\text{ V}}{104.1\text{ k}\Omega} = 0.922\text{ mA} \\ P &= I^2 R = (0.922\text{ mA})^2 100\text{ k}\Omega = 85\text{ mW} \end{aligned}$$

← b  
← c  
← d  
← e

#### Question 4

- Write the nodal equations using the general approach for the network of Fig. 8.125.
- Find the nodal voltages using determinants.
- Using the results of part (a), calculate the current through the  $20\ \Omega$  resistor.

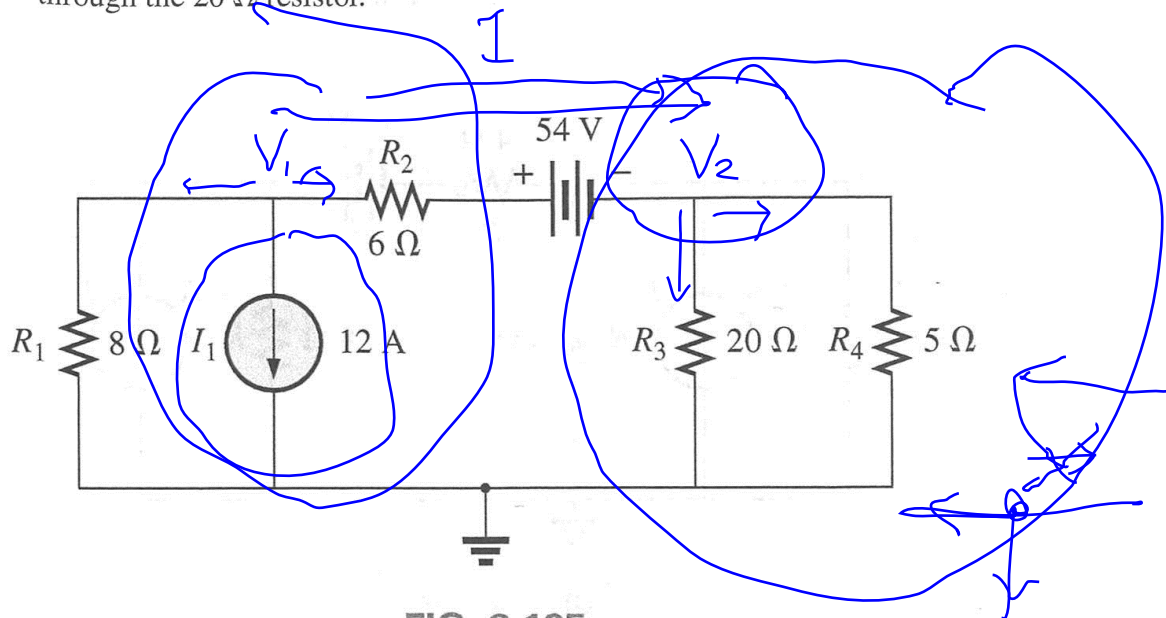


FIG. 8.125

a.  $\begin{matrix} V_1 \\ \circ \end{matrix} \quad \begin{matrix} V_2 \\ \circ \end{matrix}$

At  $V_1$ :  $\sum I_i = \sum I_o$

$$0 = \frac{V_1}{8\ \Omega} + 12\text{ A} + I_{6\Omega} \text{ and } V_1 - I_{6\Omega} - 54\text{ V} - V_2 = 0$$

$$\text{or } I = \frac{V_1 - V_2 - 54\text{ V}}{6\ \Omega} = \frac{V_1}{6\ \Omega} + \frac{V_2}{6\ \Omega} - 9\text{ A}$$

$$\text{so that } 0 = \frac{V_1}{8\ \Omega} + 12\text{ A} + \frac{V_1}{6\ \Omega} - \frac{V_2}{6\ \Omega} - 9\text{ A}$$

$$\text{or } V_1 \left[ \frac{1}{8\ \Omega} + \frac{1}{6\ \Omega} \right] - V_2 \left[ \frac{1}{6\ \Omega} \right] = -12\text{ A} + 9\text{ A} = -3\text{ A}$$

At  $V_2$ :  $\sum I_i = \sum I_o$

$$I = \frac{V_2}{20\ \Omega} + \frac{V_2}{5\ \Omega}$$

$$\text{or } \frac{V_1}{6\ \Omega} - \frac{V_2}{6\ \Omega} - 9\text{ A} = \frac{V_2}{20\ \Omega} + \frac{V_2}{5\ \Omega}$$

$$\text{and } V_2 \left[ \frac{1}{6\ \Omega} + \frac{1}{20\ \Omega} + \frac{1}{5\ \Omega} \right] - V_1 \left[ \frac{1}{6\ \Omega} \right] = -9\text{ A}$$