

ENGG104 Tutorial 4 extra Problems (revision) (Solutions)

Name_____

Student Number_____

TRUE/FALSE. Write 'T' if the statement is true and 'F' if the statement is false.

1) A Megohmmeter is an instrument for measuring very high resistance levels.

1) _____

SHORT ANSWER. Write the word or phrase that best completes each statement or answers the question.

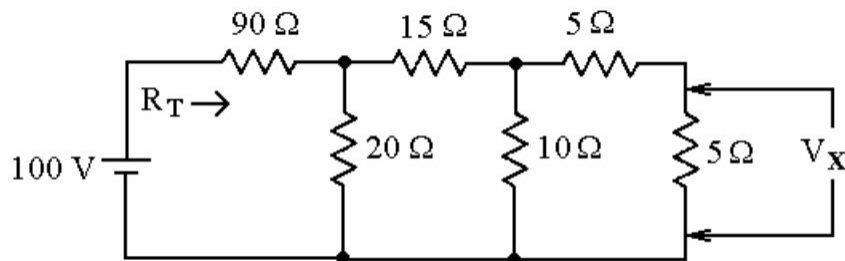


Figure 7.5

2) See Figure 7.5. Calculate V_X .

2) _____

3) See Figure 7.5. Calculate the current through the $20\ \Omega$ resistor.

3) _____

MULTIPLE CHOICE. Choose the one alternative that best completes the statement or answers the question.

4) See Figure 7.5. What is the voltage dropped across the $90\ \Omega$ resistor?

A) $90.0\ \text{V}$

B) $18.2\ \text{V}$

C) $81.8\ \text{V}$

D) $100.0\ \text{V}$

4) _____

SHORT ANSWER. Write the word or phrase that best completes each statement or answers the question.

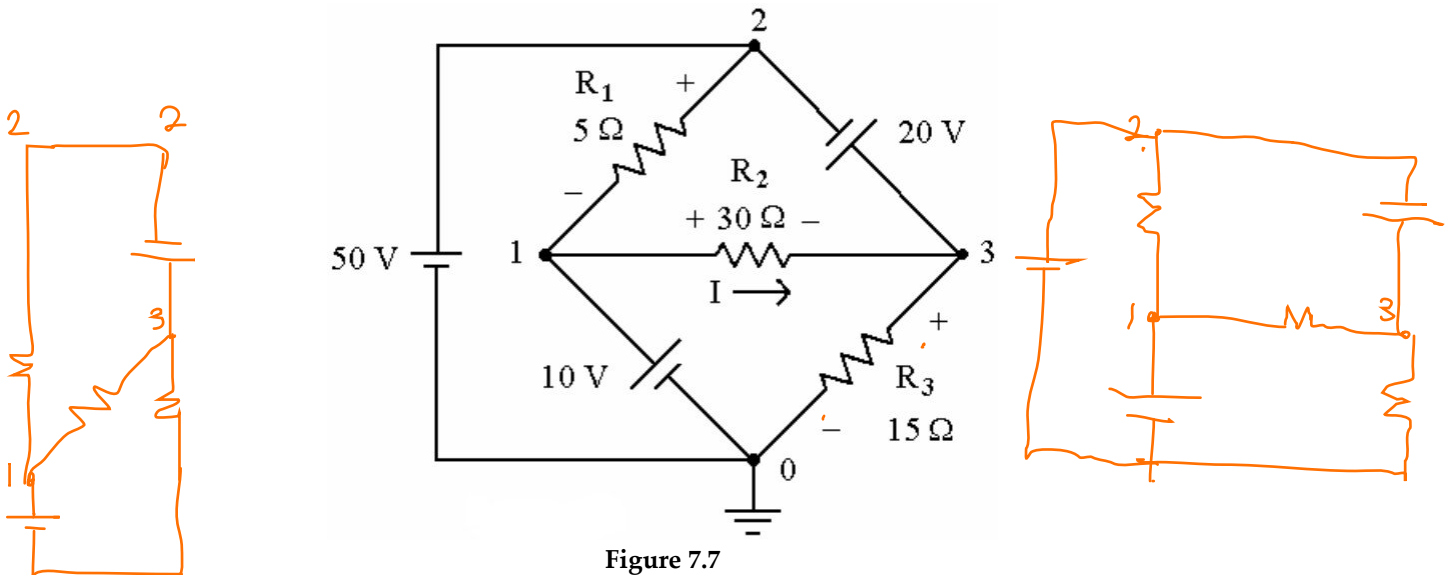


Figure 7.7

5) See Figure 7.7. Determine the current flowing through the $5\ \text{ohm}$ resistor.

5) _____

6) See Figure 7.7. Determine the power dissipated across the 15 ohm resistor.

6) _____

MULTIPLE CHOICE. Choose the one alternative that best completes the statement or answers the question.

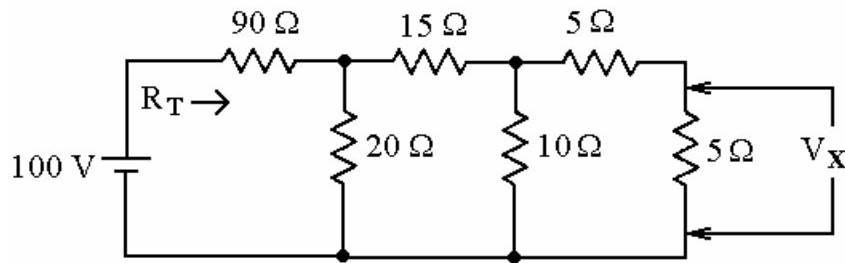


Figure 7.5

7) See Figure 7.5. What is the value of R_T ?

A) 120 Ω

B) 145 Ω

C) 100 Ω

D) 110 Ω

7) _____

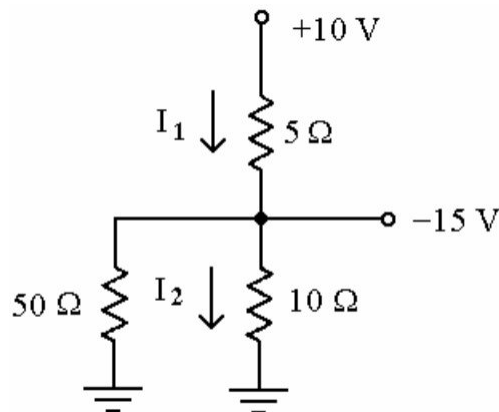


Figure 7.6

8) See Figure 7.6. What is the power dissipated across the 10 ohm resistor?

A) 22.5 watts

B) 225 watts

C) 2.25 watts

D) 0.225 watts

8) _____

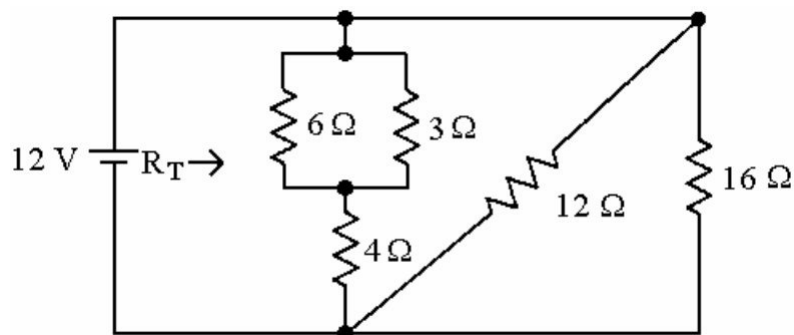


Figure 7.1

9) See Figure 7.1. What is the total resistance R_T ?

A) 6.4 Ω

B) 4.8 Ω

C) 2.4 Ω

D) 3.2 Ω

9) _____

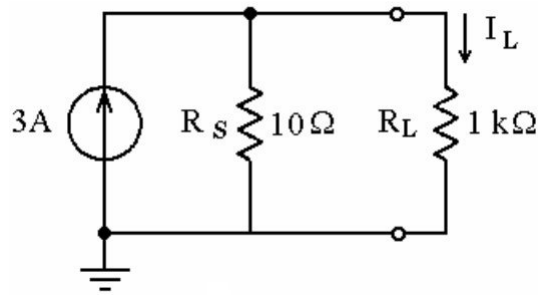


Figure 8.1

10) See Figure 8.1. What is I_L ?

A) 297.0 mA

B) 2.97 mA

C) 2.97 A

D) 29.7 mA

10) _____

SHORT ANSWER. Write the word or phrase that best completes each statement or answers the question.

11) See Figure 8.1. How much power is produced by the current source?

11) _____

12) The method of Nodal Analysis involves the use of what law?

12) _____

TRUE/FALSE. Write 'T' if the statement is true and 'F' if the statement is false.

13) An ideal current source has a $0\ \Omega$ resistance in parallel with it.

13) _____

14) Source conversions are equivalent only at their external terminals.

14) _____

SHORT ANSWER. Write the word or phrase that best completes each statement or answers the question.

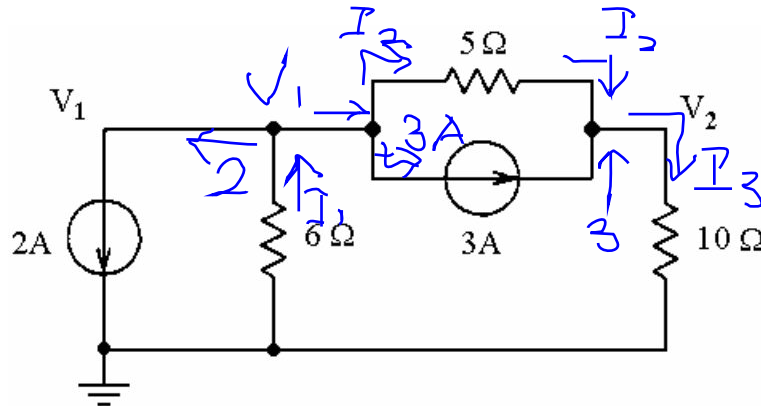


Figure 8.7

15) See Figure 8.7. Use nodal analysis to solve for voltages V_1 and V_2 .

15) _____

$$2 \quad \frac{V_1}{6}$$

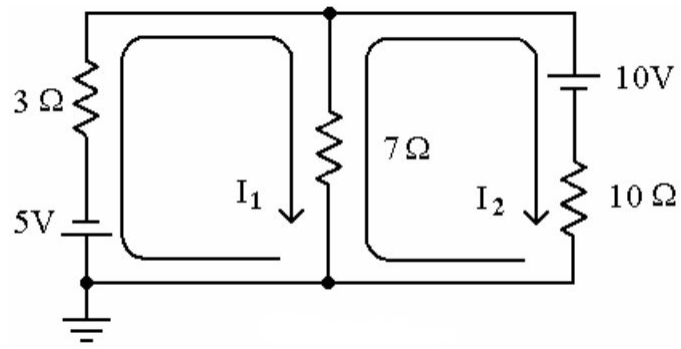


Figure 8.5

- 16) See Figure 8.5. Compute the voltages across the $3\ \Omega$, $7\ \Omega$, and $10\ \Omega$ resistors.
Use Nodal analysis

16) _____

Answer Key

Testname: ENGG104 TUT4

- 1) TRUE
- 2) 1.25 V
- 3) 0.5 A
- 4) A
- 5) 8 amps
- 6) 326.7 watts
- 7) C
- 8) A
- 9) D
- 10) D
- 11) 89.1 watts
- 12) Kirchhoff's Current law
- 13) FALSE
- 14) TRUE
- 15) $V_1 = -12.9 \text{ V}$, $V_2 = 1.43 \text{ V}$
- 16) $+3.84 \text{ V}$, -1.16 V , -11.16 V (polarity referenced from top to bottom)