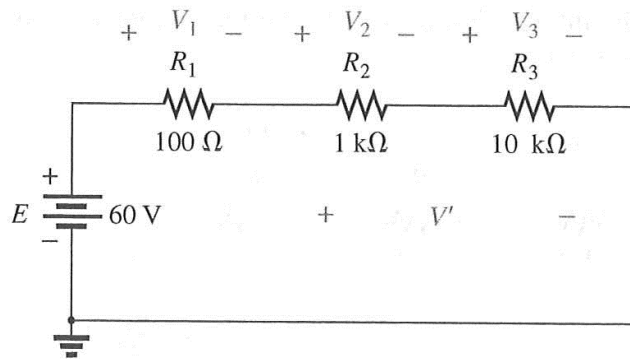


# ENGG104 Tutorial 3 Class Questions

Team Name: \_\_\_\_\_

## Question 1 [common exam question]

Determine  $V_1, V_2, V_3$  and  $V'$ . [Voltage Divider]




- a. ~~scribbled out~~
- b.  $V_3: V_2 = 10\text{ k}\Omega:1\text{ k}\Omega = 10:1$   
 $V_3: V_1 = 10\text{ k}\Omega:100\text{ }\Omega = 100:1$
- c.  $V_3 = \frac{R_3 E}{R_T} = \frac{(10\text{ k}\Omega)(60\text{ V})}{0.1\text{ k}\Omega + 1\text{ k}\Omega + 10\text{ k}\Omega} = 54.05\text{ V}$
- d.  $V' = \frac{(R_2 + R_3)E}{R_T} = \frac{(1\text{ k}\Omega + 10\text{ k}\Omega)(60\text{ V})}{11.1\text{ k}\Omega} = 59.46\text{ V}$

c  $V_2 = 5.41\text{ V}$

$V_1 = 0.54\text{ V}$

## Question 2 [common exam question]

Determine  $V_1$  and  $V_2$

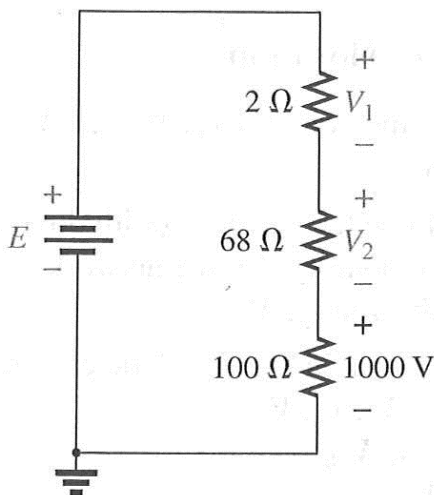

$100\text{ }\Omega \rightarrow 1000\text{ V}$   
 $68\text{ }\Omega \rightarrow \frac{1000}{100} \times 68$   
 $2\text{ }\Omega \rightarrow \frac{1000}{100} \times 2$

c.  $\frac{1000\text{ V}}{100\text{ }\Omega} = \frac{V_2}{68\text{ }\Omega}, V_2 = \frac{68\text{ }\Omega(1000\text{ V})}{100\text{ }\Omega} = 680\text{ V}$   
 $\frac{1000\text{ V}}{100\text{ }\Omega} = \frac{V_1}{2\text{ }\Omega}, V_1 = \frac{2\text{ }\Omega(1000\text{ V})}{100\text{ }\Omega} = 20\text{ V}$   
 $E = V_1 + V_2 + 1000\text{ V}$   
 $= 20\text{ V} + 680\text{ V} + 1000\text{ V}$   
 $= 1700\text{ V}$

d  
b


### Question 3

Estimate the total resistance without any calculation: \_\_\_\_\_

Calculate the total resistance  $R_T$  and compare :


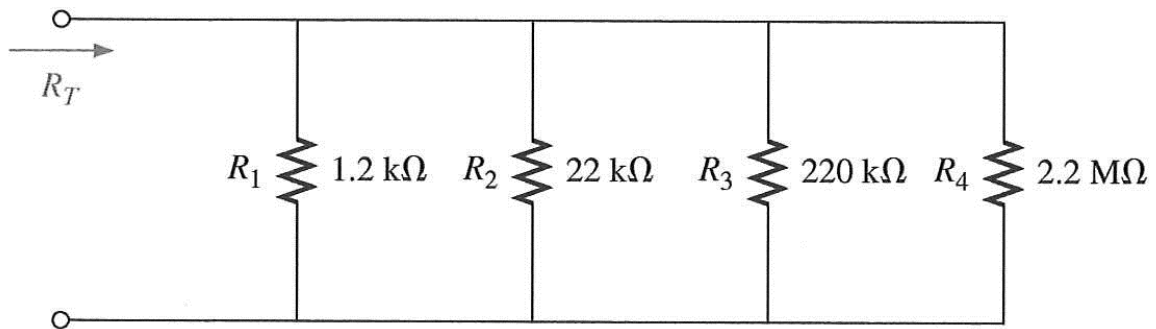
$$\frac{2 \times 4}{2 + 4} = \frac{8}{6} = \frac{4}{3}$$




- a. 1.2 kΩ
- b. about 1 kΩ

$$\begin{aligned} \text{c. } R_T &= \frac{1}{\frac{1}{1.2 \text{ k}\Omega} + \frac{1}{22 \text{ k}\Omega} + \frac{1}{220 \text{ k}\Omega} + \frac{1}{2.2 \text{ M}\Omega}} \\ &= \frac{1}{833.333 \times 10^{-6} \text{ S} + 45.455 \times 10^{-6} \text{ S} + 4.545 \times 10^{-6} \text{ S} + 0.455 \times 10^{-6} \text{ S}} \\ &= \frac{1}{883.788 \times 10^{-6} \text{ S}} = 1.131 \text{ k}\Omega \end{aligned}$$

*Handwritten blue checkmark*
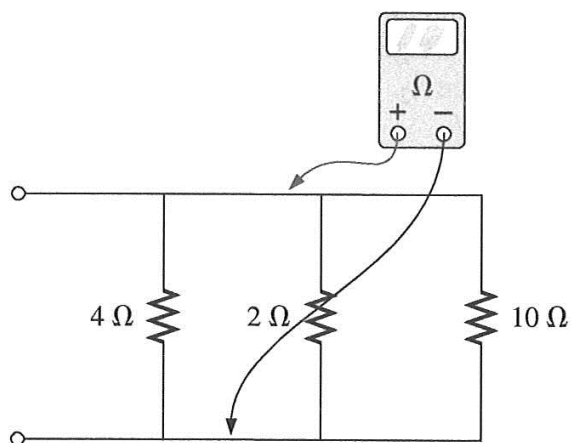
### Question 4

What is the ohmmeter reading for each configuration in Fig. 77?



$$\text{a. } R_T = \frac{1}{\frac{1}{4 \Omega} + \frac{1}{2 \Omega} + \frac{1}{10 \Omega}} = \frac{1}{0.25 \text{ S} + 0.50 \text{ S} + 0.10 \text{ S}} = \frac{1}{0.85 \text{ S}} = 1.18 \Omega$$

### Question 5 [Typical exam question]

For the parallel network in Fig. 79:

- Find the total resistance.
- What is the voltage across each branch?
- Determine the source current and the current through each branch.
- Verify that the source current equals the sum of the branch currents.

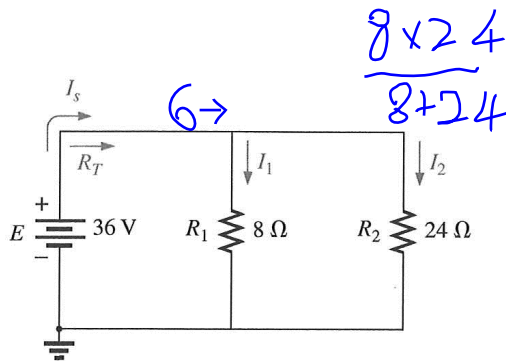


FIG. 79

- 9.
- $R_T = \frac{(8\ \Omega)(24\ \Omega)}{8\ \Omega + 24\ \Omega} = 6\ \Omega$  a
  - $V_{R_1} = V_{R_2} = 36\ \text{V}$
  - $I_s = \frac{E}{R_T} = \frac{36\ \text{V}}{6\ \Omega} = 6\ \text{A}$  b  
 $I_1 = \frac{V_{R_1}}{R_1} = \frac{36\ \text{V}}{8\ \Omega} = 4.5\ \text{A}$  c  
 $I_2 = \frac{V_{R_2}}{R_2} = \frac{36\ \text{V}}{24\ \Omega} = 1.5\ \text{A}$  d
  - $I_s = I_1 + I_2$   
 $6\ \text{A} = 4.5\ \text{A} + 1.5\ \text{A} = 6\ \text{A}$  (checks)

### Question 6 [Past exam Question]

10. For the network of Fig. 80:

- Find the current through each branch.
- Find the total resistance.
- Calculate  $I_s$  using the result of part (b).
- Find the source current using the result of part (a).
- Compare the results of parts (c) and (d).

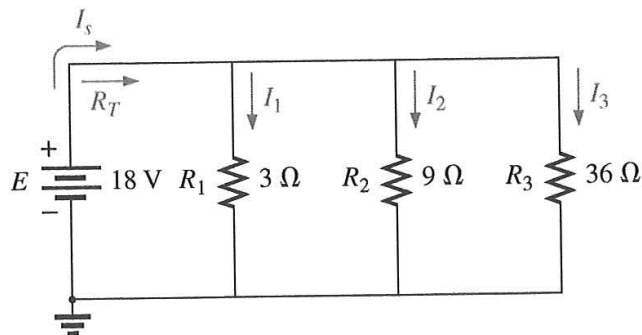


FIG. 80

Problem 10.


10. a.  $I_1 = \frac{V_{R_1}}{R_1} = \frac{18 \text{ V}}{3 \Omega} = 6 \text{ A}, I_2 = \frac{V_{R_2}}{R_2} = \frac{18 \text{ V}}{9 \Omega} = 2 \text{ A}, I_3 = \frac{V_{R_3}}{R_3} = \frac{18 \text{ V}}{36 \Omega} = 0.5 \text{ A}$

b.  $R_T = \frac{1}{\frac{1}{3 \Omega} + \frac{1}{9 \Omega} + \frac{1}{36 \Omega}} = \frac{1}{0.333 \text{ S} + 0.111 \text{ S} + 0.028 \text{ S}}$   
 $= \frac{1}{472 \times 10^{-3} \text{ S}} = 2.12 \Omega$

c.  $I_s = \frac{E}{R_T} = \frac{18 \text{ V}}{2.12 \Omega} = 8.5 \text{ A}$

**Question 7 [current divider]**

31. a. Determine one of the unknown currents of Fig. 100 using the current divider rule.  
 b. Determine the other current using Kirchhoff's current law.

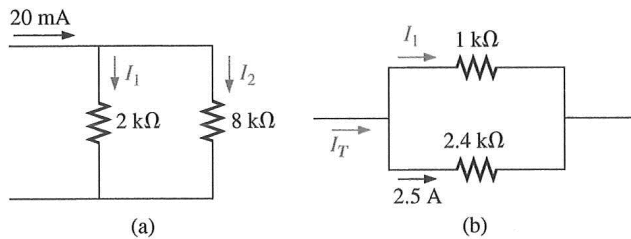


**FIG. 100**  
 Problem 31.

31. a.  $I_1 = \frac{8 \text{ k}\Omega(20 \text{ mA})}{2 \text{ k}\Omega + 8 \text{ k}\Omega} = 16 \text{ mA}$   
 $I_2 = 20 \text{ mA} - 16 \text{ mA} = 4 \text{ mA}$

b.  $I_{2.4 \text{ k}\Omega} = 2.5 \text{ A} = \frac{1 \text{ k}\Omega(I_T)}{1 \text{ k}\Omega + 2.4 \text{ k}\Omega} = \frac{1 \text{ k}\Omega(I_T)}{3.4 \text{ k}\Omega}$   
 and  $I_T = \frac{3.4 \text{ k}\Omega(2.5 \text{ A})}{1 \text{ k}\Omega} = 8.5 \text{ A}$   
 $I_1 = I_T - 2.5 \text{ A} = 8.5 \text{ A} - 2.5 \text{ A} = 6 \text{ A}$

### Question 8 [typical exam question]

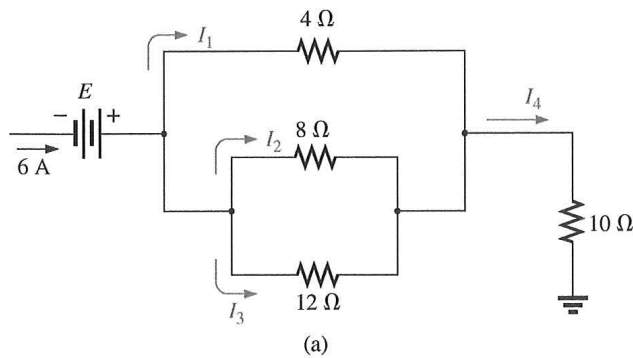32. For each network of Fig. 101, determine the unknown currents.



$$\begin{aligned}
 32. \quad a. \quad R_T &= \frac{1}{\frac{1}{4 \, \Omega} + \frac{1}{8 \, \Omega} + \frac{1}{12 \, \Omega}} = \frac{1}{250 \times 10^{-3} \text{ S} + 125 \times 10^{-3} \text{ S} + 83.333 \times 10^{-3} \text{ S}} \\
 &= \frac{1}{458.333 \times 10^{-3}} = 2.18 \, \Omega \\
 I_x &= \frac{R_T}{R_x} I, \quad I_1 = \frac{2.18 \, \Omega}{4 \, \Omega} (6 \text{ A}) = \mathbf{3.27 \text{ A}} \\
 I_2 &= \frac{2.18 \, \Omega}{8 \, \Omega} (6 \text{ A}) = \mathbf{1.64 \text{ A}} \\
 I_3 &= \frac{2.18 \, \Omega}{12 \, \Omega} (6 \text{ A}) = \mathbf{1.09 \text{ A}} \\
 I_4 &= \mathbf{6 \text{ A}}
 \end{aligned}$$

a  
b  
c  
d  
e

### Question 9 [Past exam question]

Will the breaker trip??

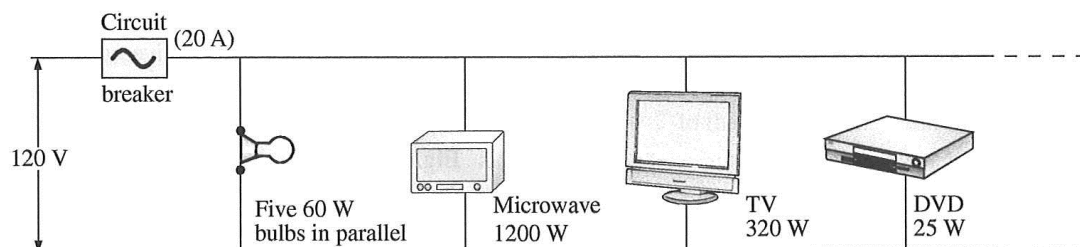


FIG. 91

$$P = IV$$

$$I = \frac{P}{V}$$

a.  $5 \times 60 \text{ W} = 300 \text{ W}$

$$I_{\text{bulbs}} = \frac{300 \text{ W}}{120 \text{ V}} = \mathbf{2.5 \text{ A}}$$

$$I_{\text{micro}} = \frac{1200 \text{ W}}{120 \text{ V}} = \mathbf{10 \text{ A}}$$

$$I_{\text{TV}} = \frac{320 \text{ W}}{120 \text{ V}} = \mathbf{2.67 \text{ A}}$$

$$I_{\text{DVD}} = \frac{25 \text{ W}}{120 \text{ V}} = \mathbf{208.33 \text{ mA}}$$

a

b

c

d

b.  $I_s = \sum I = 2.5 \text{ A} + 10 \text{ A} + 2.67 \text{ A} + 208.33 \text{ mA} = \mathbf{15.38 \text{ A}}$

**No**

—