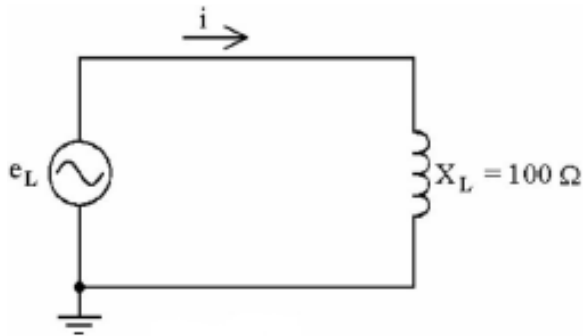


Attribution Nidhal Abdulaziz

Tutorial 9 additional solutions

Question 1




Tut week 10 on-line Tut  
Q.1



$$e_L = 50 \sin(50t + 20^\circ) \text{ V}$$

A hand-drawn circuit diagram showing an AC voltage source  $e_L$  connected in series with an inductor with reactance  $X_L = 100 \Omega$ .

$$i = \frac{e}{X_L} = \frac{50 \angle 20^\circ}{100 \angle +90^\circ} = 0.5 \text{ A} \angle -70^\circ$$

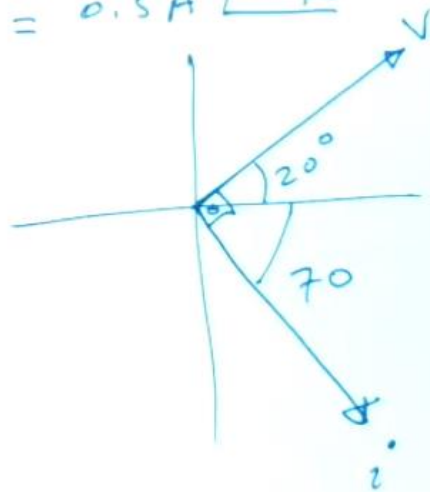

Question 16

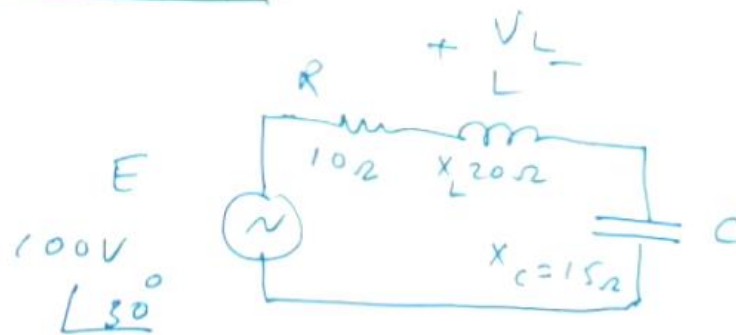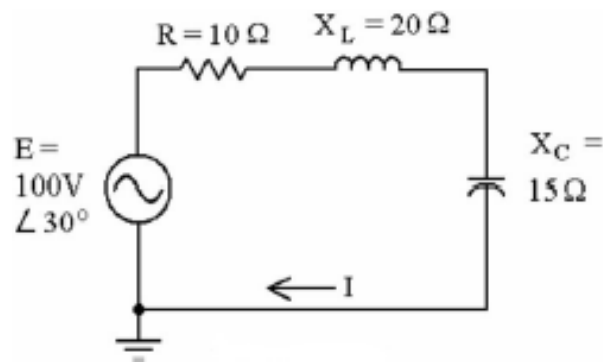


$$V_L = E \times \frac{X_L}{R + jX_L - jX_C}$$

$$V_L = \frac{100V \angle 30^\circ \times 20 \angle +90^\circ}{10 + j20 - j15}$$

$$V_L = \frac{2000 \angle 120^\circ}{10 + j5}$$

$$V_L = \frac{2000 \angle 120^\circ}{11.18 \angle 26.5^\circ} = 178.9V \angle 93.5^\circ$$

Question 20

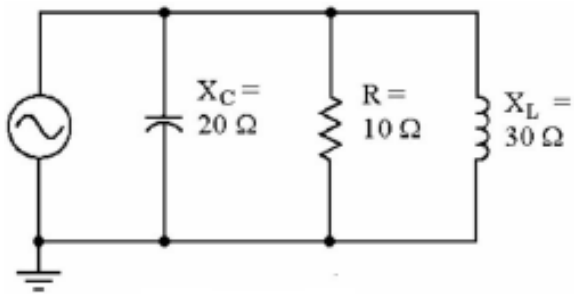

Q. 20      on-line Tut.




$$G = \frac{1}{R} = \frac{1}{10} = 0.1\ S \angle 0^\circ$$

$$B_L = \frac{1}{X_L} = \frac{1}{30} = 0.033\ S \angle -90^\circ$$

$$B_C = \frac{1}{X_C} = \frac{1}{20} = 0.05\ S \angle +90^\circ$$

$$Y = G + B_L + B_C$$

=

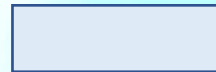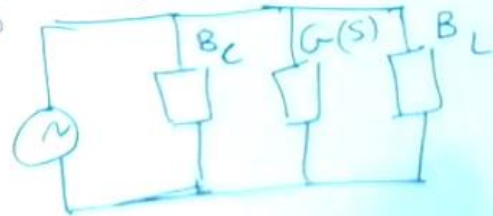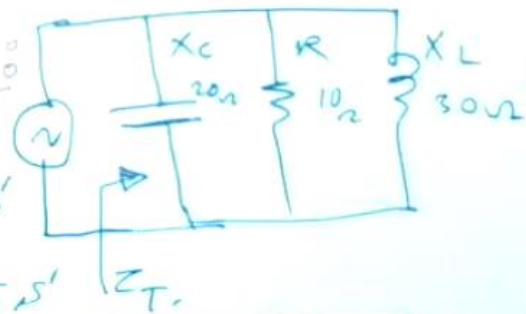

$$Y = G - jB_L + jB_C$$

$$Y = 0.01 - j0.03 + j0.05$$

$$Y = 0.01 + j0.017$$

$$|Y| = \sqrt{(0.01)^2 + (0.017)^2} = 0.019 \text{ S}$$


$$\theta_Y = \tan^{-1}\left(\frac{0.017}{0.01}\right) = 59.53^\circ$$

$$Y_T = 0.019 \text{ S} \angle 59.53^\circ$$

$$Z_T = \frac{1}{Y} = \frac{1}{0.019} \angle -59.53^\circ$$

$$Z_T = 52.60 \Omega \angle -59.53^\circ$$


Question 31

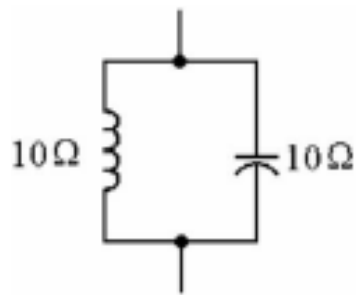

Tut week 10

Q. 31

$$Z_T = ?$$

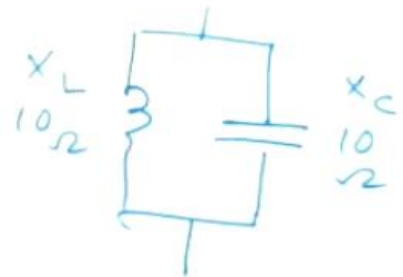


$$Z_T = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2} \rightarrow Z_T = \frac{10 \angle 90^\circ \times 10 \angle -90^\circ}{j10 - j10}$$

$$Z_T = \infty$$


$$Y_t = Y_1 + Y_2$$

$$Z_T = \frac{1}{Y_t}$$

Question 34

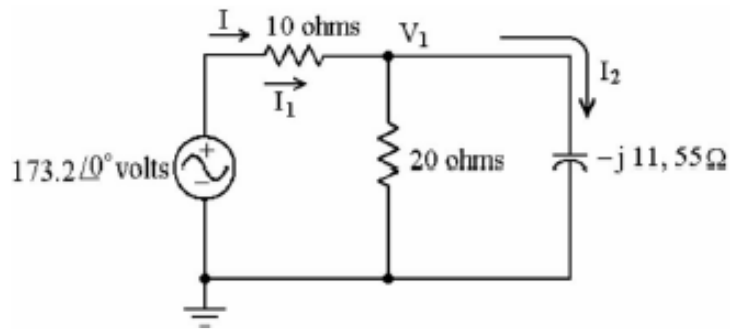

$$I = \frac{V_{in}}{Z_T}$$

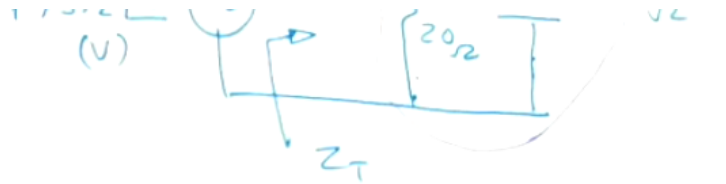

$$Z_T = 10 \Omega + Z'$$

$$Z' = \frac{20 \angle 0^\circ \times (11.55 \angle -90^\circ)}{20 - j 11.55} = \frac{20 \times 11.55 \angle -90^\circ}{23 \angle -30^\circ}$$


$$Z' = 10 \angle -60^\circ (\Omega)$$

$$Z_T = 10 + [10 \cos(-60^\circ) + j 10 \sin(-60^\circ)]$$

$$Z_T = ( ) \angle$$

$$I = \frac{173.2 \angle 0^\circ}{Z_T}$$

Question 38

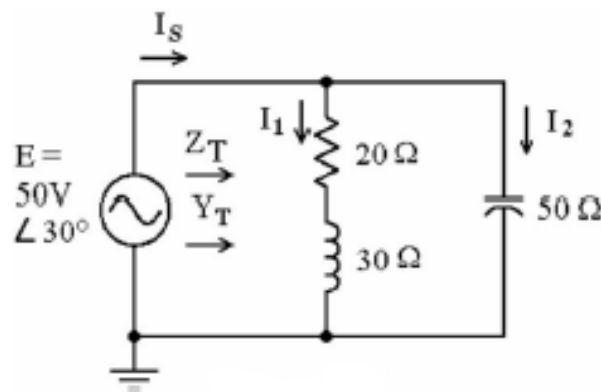


Week 10

On-line Tut

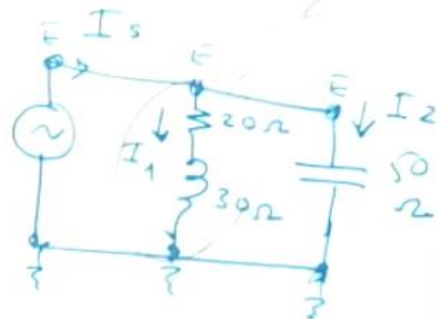Q. 38

$$I_2 = \frac{E}{X_C}$$

$$I_2 = \frac{50V \angle 30^\circ}{50\Omega \angle -90^\circ} = 1A \angle 120^\circ$$



$$I_1 = \frac{E}{Z'} = \frac{50V \angle 30^\circ}{20 + j30} = \frac{50 \angle 30^\circ}{36 \angle 56.3^\circ}$$

$$I_1 = \underline{\underline{1.38 \text{ A} \angle -26.3^\circ}}$$

$$I_s = I_1 + I_2$$

$$= 1.38 \angle -26.3^\circ + 1 \angle 120^\circ$$

$$I_s = 1.38 [\cos(-26.3^\circ) + j \sin(-26.3^\circ)] \\ + 1 [\cos(120^\circ) + j \sin(120^\circ)]$$

$$I_s = R_e + j I_m.$$


---