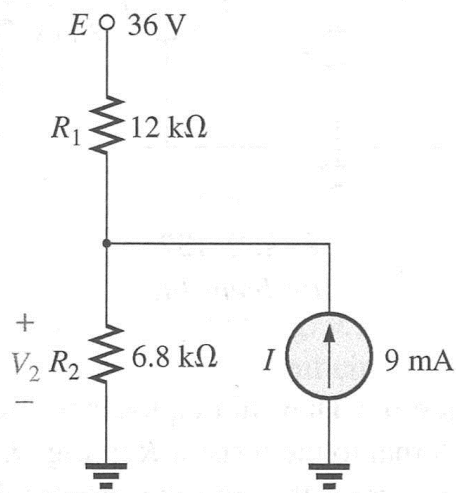


ENGG104 Tutorial 5 Class Questions

Team Name: _____

Question 1 [typical exam question]

Using superposition, find the voltage V_2 for the network in Fig. 9.123.

**FIG. 9.123**

Question 2

- a. Find the Thévenin equivalent circuit for the network external to the resistor R in Fig. 9.126.
- b. Find the current through R when R is $2\ \Omega$, $30\ \Omega$, and $100\ \Omega$.

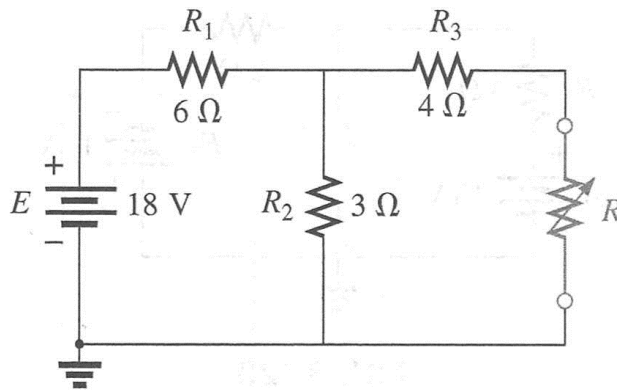


FIG. 9.126

Question 3 [typical exam question]

- a. Find the Thévenin equivalent circuit for the network external to the resistor R for the network in Fig. 9.127.
- b. Find the power delivered to R when R is $2\text{ k}\Omega$ and $100\text{ k}\Omega$.

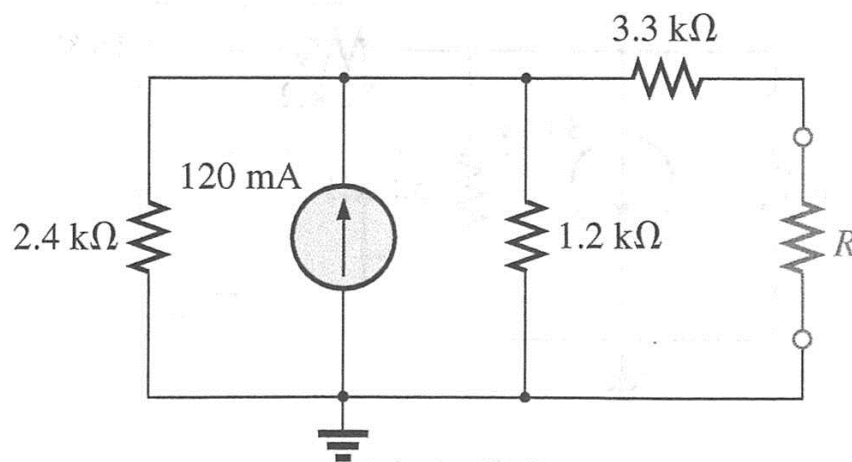


FIG. 9.127

Question 4

- Write the nodal equations using the general approach for the network of Fig. 8.125.
- Find the nodal voltages using determinants.
- Using the results of part (a), calculate the current through the $20\ \Omega$ resistor.

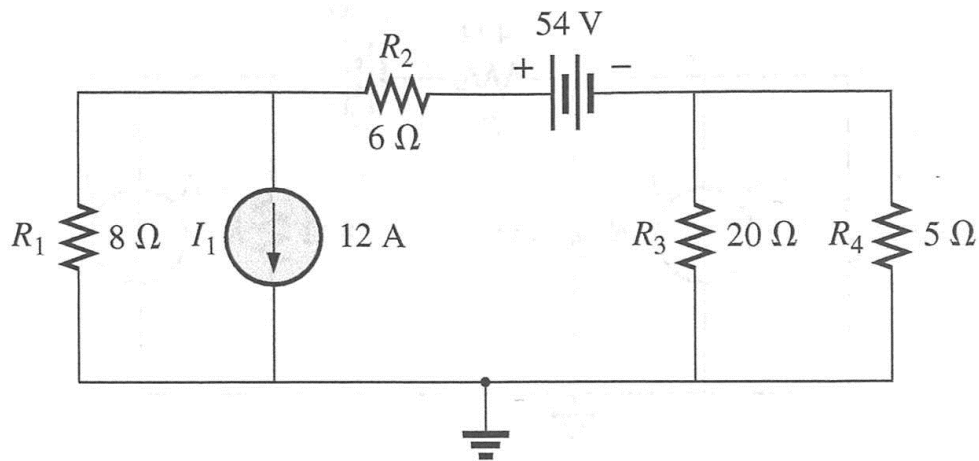


FIG. 8.125