

ENGG104 Tutorial 4 Class Questions

Team Name: _____

Question 1

Which resistors are in series and which are in parallel?

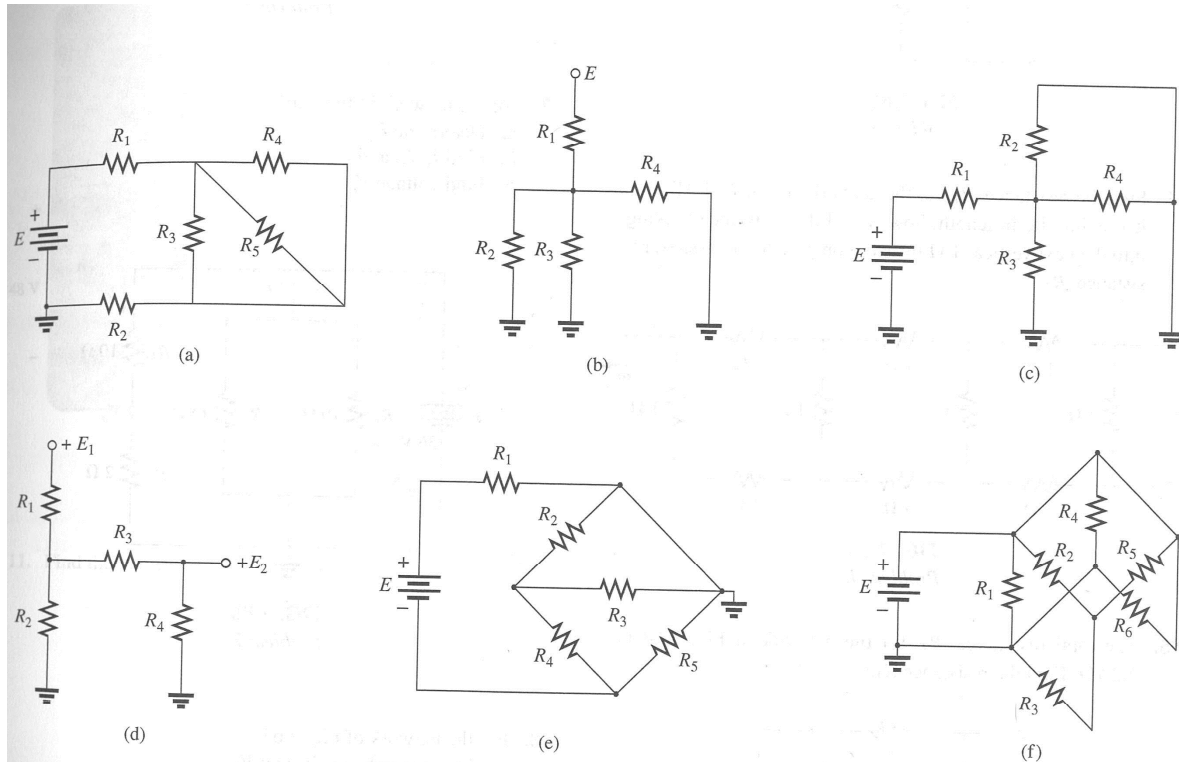


FIG. 7.60
Problem 1.

Question 2 [Past exam question]

For the network in Fig. 7.71:

- Find currents I_s , I_2 , and I_6 .
- Find voltages V_1 and V_5 .
- Find the power delivered to the $3\text{ k}\Omega$ resistor.

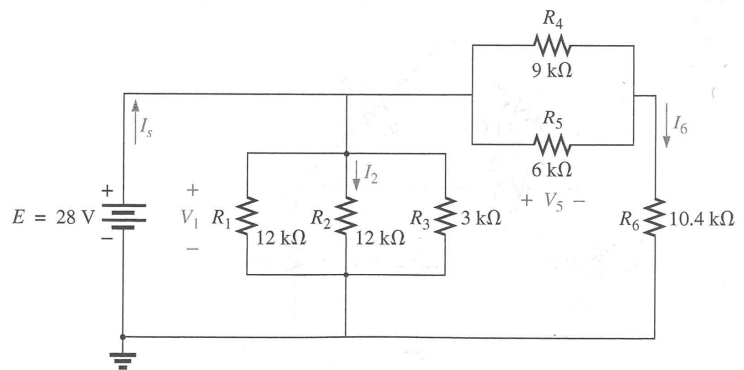


FIG. 7.71

Question 3

8. Convert the current sources in Fig. 8.104 to voltage sources.

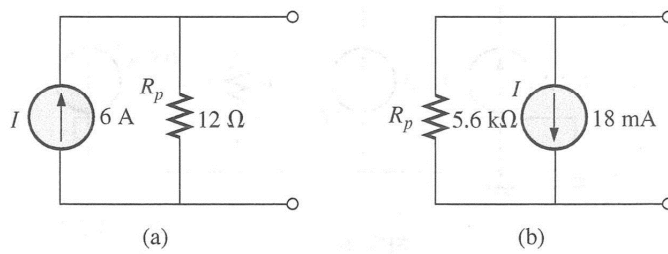


FIG. 8.104

Question 4 [typical exam question]

6. For the network in Fig. 8.102:
- Find the currents I_1 and I_s .
 - Find the voltages V_s and V_3 .

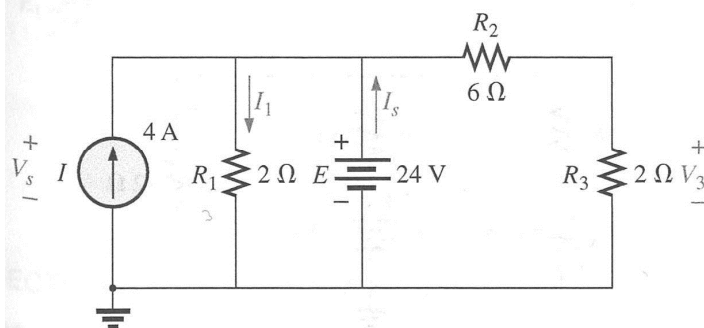


FIG. 8.102

Problem 6.

Question 5 [Typical exam question]

42. a. Write the nodal equations using the general approach for the network of Fig. 8.126.
- b. Find the nodal voltages using determinants.
- c. What is the total power supplied by the current sources?

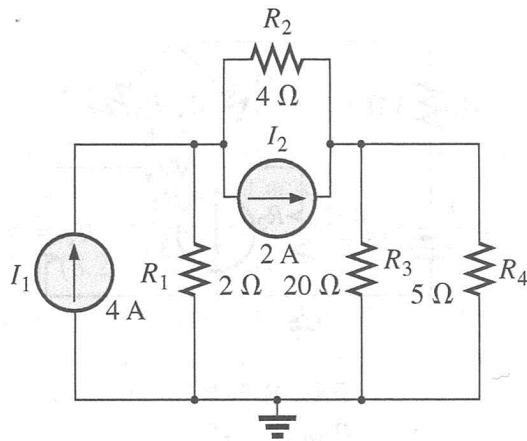


FIG. 8.126