

# ENGG104 Tutorial 4 extra Problems (revision)

Name\_\_\_\_\_

Student Number\_\_\_\_\_

**TRUE/FALSE.** Write 'T' if the statement is true and 'F' if the statement is false.

1) A Megohmmeter is an instrument for measuring very high resistance levels.

1) \_\_\_\_\_

**SHORT ANSWER.** Write the word or phrase that best completes each statement or answers the question.

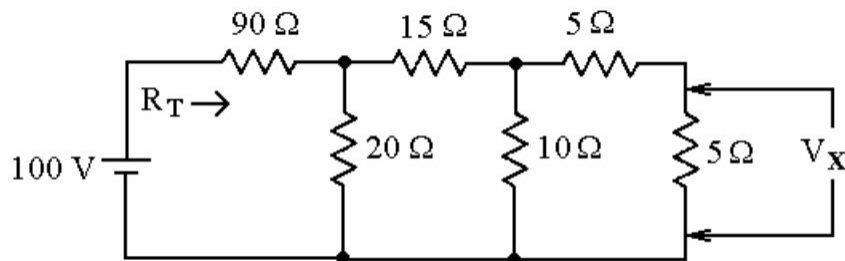


Figure 7.5

2) See Figure 7.5. Calculate  $V_X$ .

2) \_\_\_\_\_

3) See Figure 7.5. Calculate the current through the  $20\ \Omega$  resistor.

3) \_\_\_\_\_

**MULTIPLE CHOICE.** Choose the one alternative that best completes the statement or answers the question.

4) See Figure 7.5. What is the voltage dropped across the  $90\ \Omega$  resistor?

A) 90.0 V

B) 18.2 V

C) 81.8 V

D) 100.0 V

4) \_\_\_\_\_

**SHORT ANSWER.** Write the word or phrase that best completes each statement or answers the question.

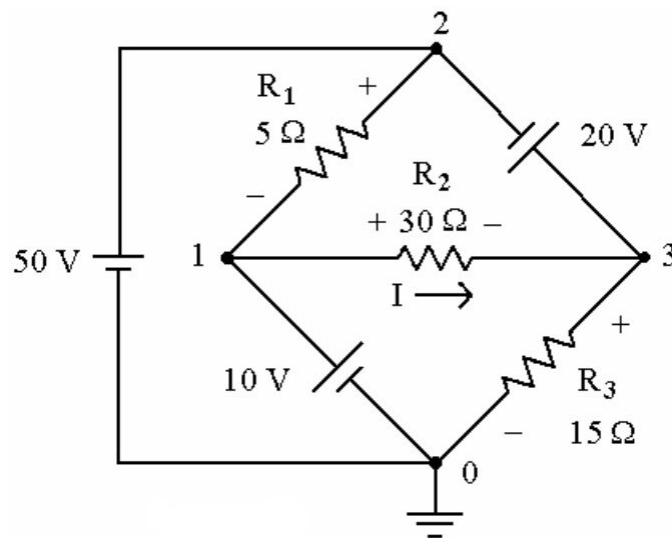


Figure 7.7

5) See Figure 7.7. Determine the current flowing through the 5 ohm resistor.

5) \_\_\_\_\_

6) See Figure 7.7. Determine the power dissipated across the 15 ohm resistor.

6) \_\_\_\_\_

**MULTIPLE CHOICE.** Choose the one alternative that best completes the statement or answers the question.

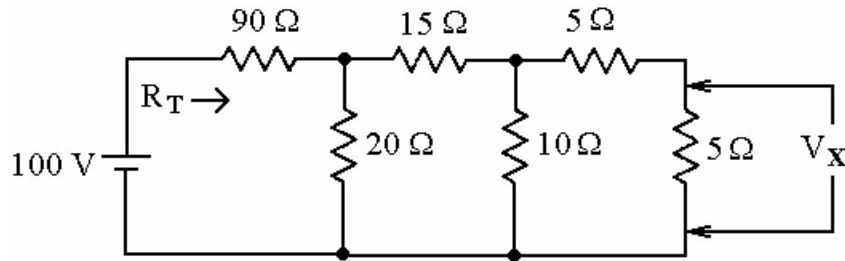


Figure 7.5

7) See Figure 7.5. What is the value of  $R_T$ ?

A) 120  $\Omega$

B) 145  $\Omega$

C) 100  $\Omega$

D) 110  $\Omega$

7) \_\_\_\_\_

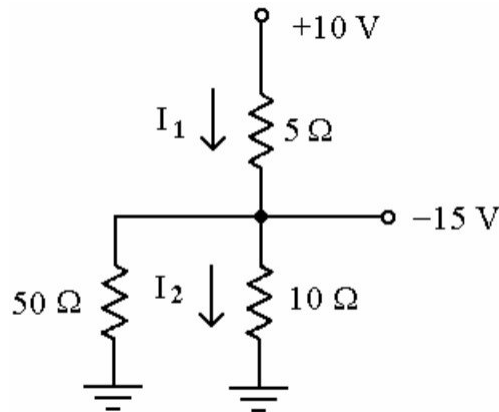


Figure 7.6

8) See Figure 7.6. What is the power dissipated across the 10 ohm resistor?

A) 22.5 watts

B) 225 watts

C) 2.25 watts

D) 0.225 watts

8) \_\_\_\_\_

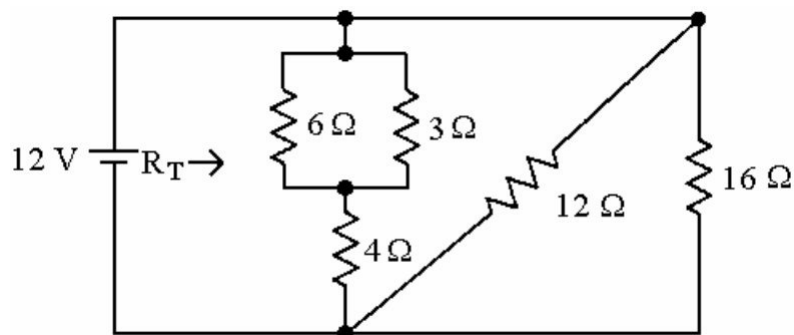


Figure 7.1

9) See Figure 7.1. What is the total resistance  $R_T$ ?

A) 6.4  $\Omega$

B) 4.8  $\Omega$

C) 2.4  $\Omega$

D) 3.2  $\Omega$

9) \_\_\_\_\_

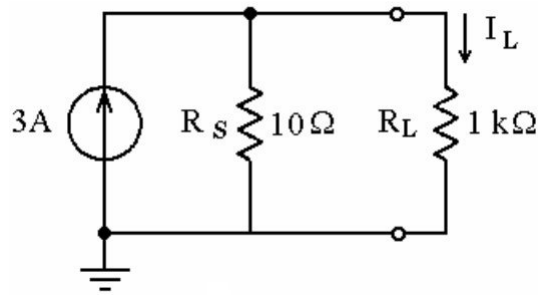


Figure 8.1

10) See Figure 8.1. What is  $I_L$ ?

A) 297.0 mA

B) 2.97 mA

C) 2.97 A

D) 29.7 mA

10) \_\_\_\_\_

**SHORT ANSWER. Write the word or phrase that best completes each statement or answers the question.**

11) See Figure 8.1. How much power is produced by the current source?

11) \_\_\_\_\_

12) The method of Nodal Analysis involves the use of what law?

12) \_\_\_\_\_

**TRUE/FALSE. Write 'T' if the statement is true and 'F' if the statement is false.**

13) An ideal current source has a  $0\ \Omega$  resistance in parallel with it.

13) \_\_\_\_\_

14) Source conversions are equivalent only at their external terminals.

14) \_\_\_\_\_

**SHORT ANSWER. Write the word or phrase that best completes each statement or answers the question.**

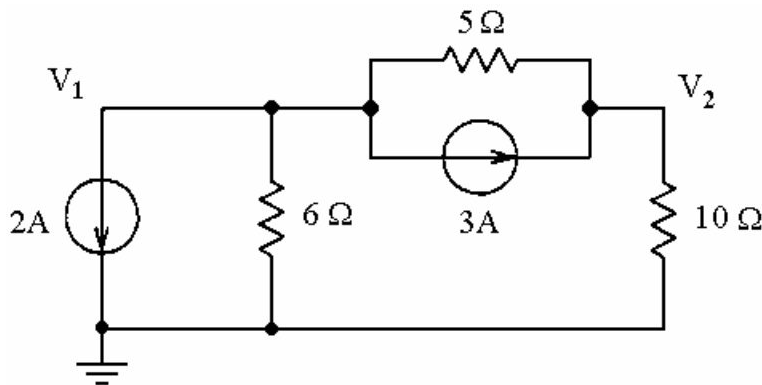


Figure 8.7

15) See Figure 8.7. Use nodal analysis to solve for voltages  $V_1$  and  $V_2$ .

15) \_\_\_\_\_

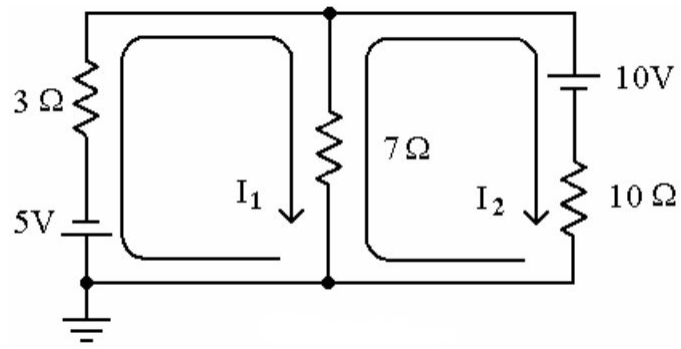


Figure 8.5

- 16) See Figure 8.5. Compute the voltages across the  $3\ \Omega$ ,  $7\ \Omega$ , and  $10\ \Omega$  resistors.  
Use Nodal analysis

16) \_\_\_\_\_