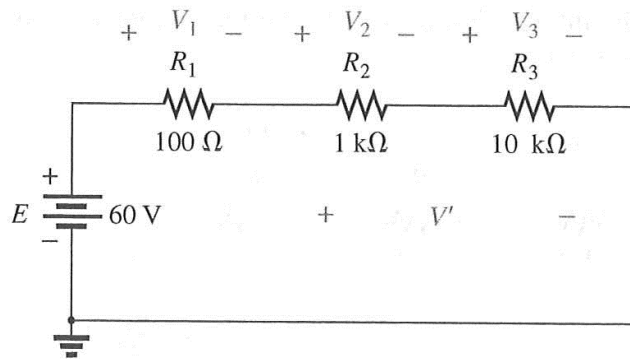


ENGG104 Tutorial 3 Class Questions

Team Name: _____


Question 1 [common exam question]

Determine V_1, V_2, V_3 and V' . [Voltage Divider]



Question 2 [common exam question]


Determine V_1 and V_2

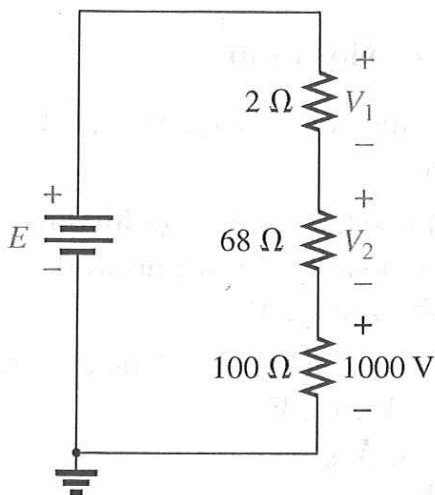

Question 3


Estimate the total resistance without any calculation: _____

Calculate the total resistance R_T and compare :

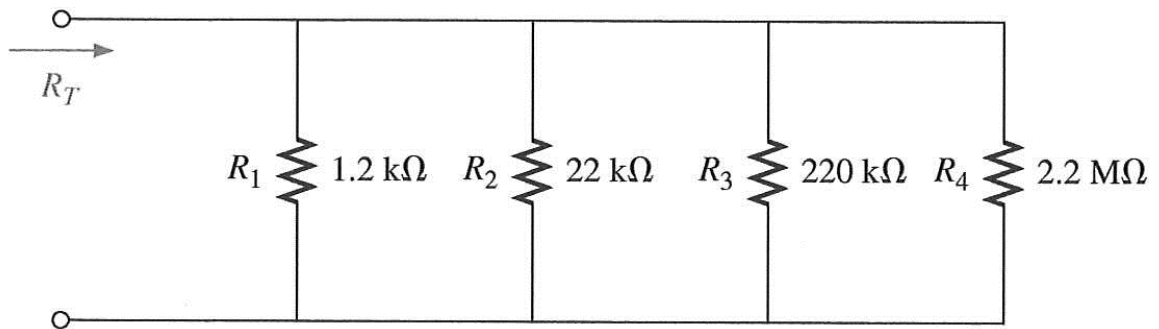

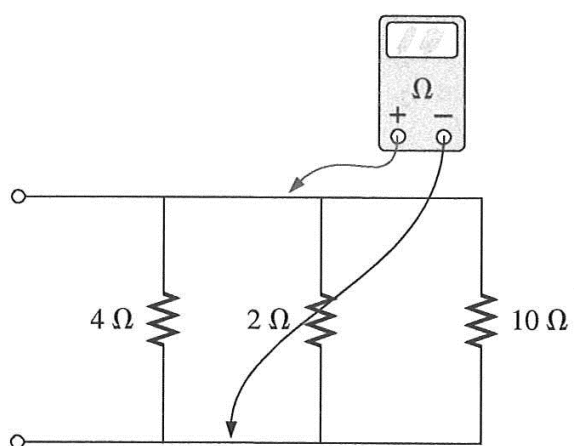Question 4

What is the ohmmeter reading for each configuration in Fig. 77?



Question 5 [Typical exam question]

For the parallel network in Fig. 79:

- Find the total resistance.
- What is the voltage across each branch?
- Determine the source current and the current through each branch.
- Verify that the source current equals the sum of the branch currents.

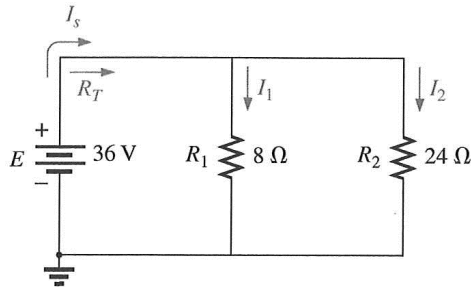


FIG. 79

Question 6 [Past exam Question]

10. For the network of Fig. 80:

- Find the current through each branch.
- Find the total resistance.
- Calculate I_s using the result of part (b).
- Find the source current using the result of part (a).
- Compare the results of parts (c) and (d).

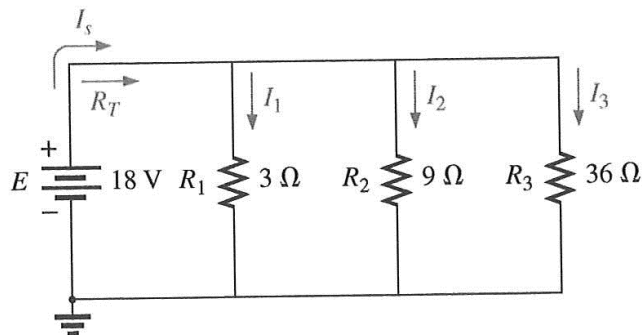


FIG. 80

Problem 10.

Question 7 [current divider]

31. a. Determine one of the unknown currents of Fig. 100 using the current divider rule.
b. Determine the other current using Kirchhoff's current law.


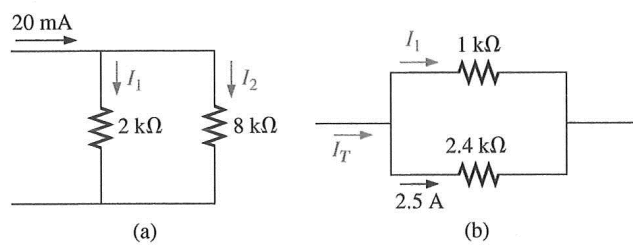


FIG. 100
Problem 31.

Question 8 [typical exam question]

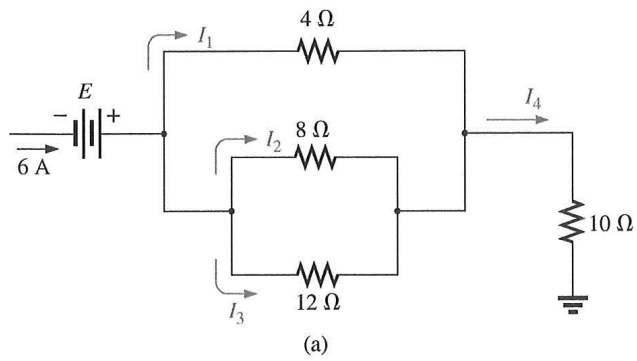32. For each network of Fig. 101, determine the unknown currents.



Question 9 [Past exam question]

Will the breaker trip??

