


ENGG104 Tutorial 11 Class Questions [past exam questions]

Team Name: _____

QUESTION 1 -


Determine the equivalent resistance, R_{eq} , looking in at terminals marked a and b when:

- (a) terminals c and d are open circuited, and
- (b) terminals c and d are short circuited.

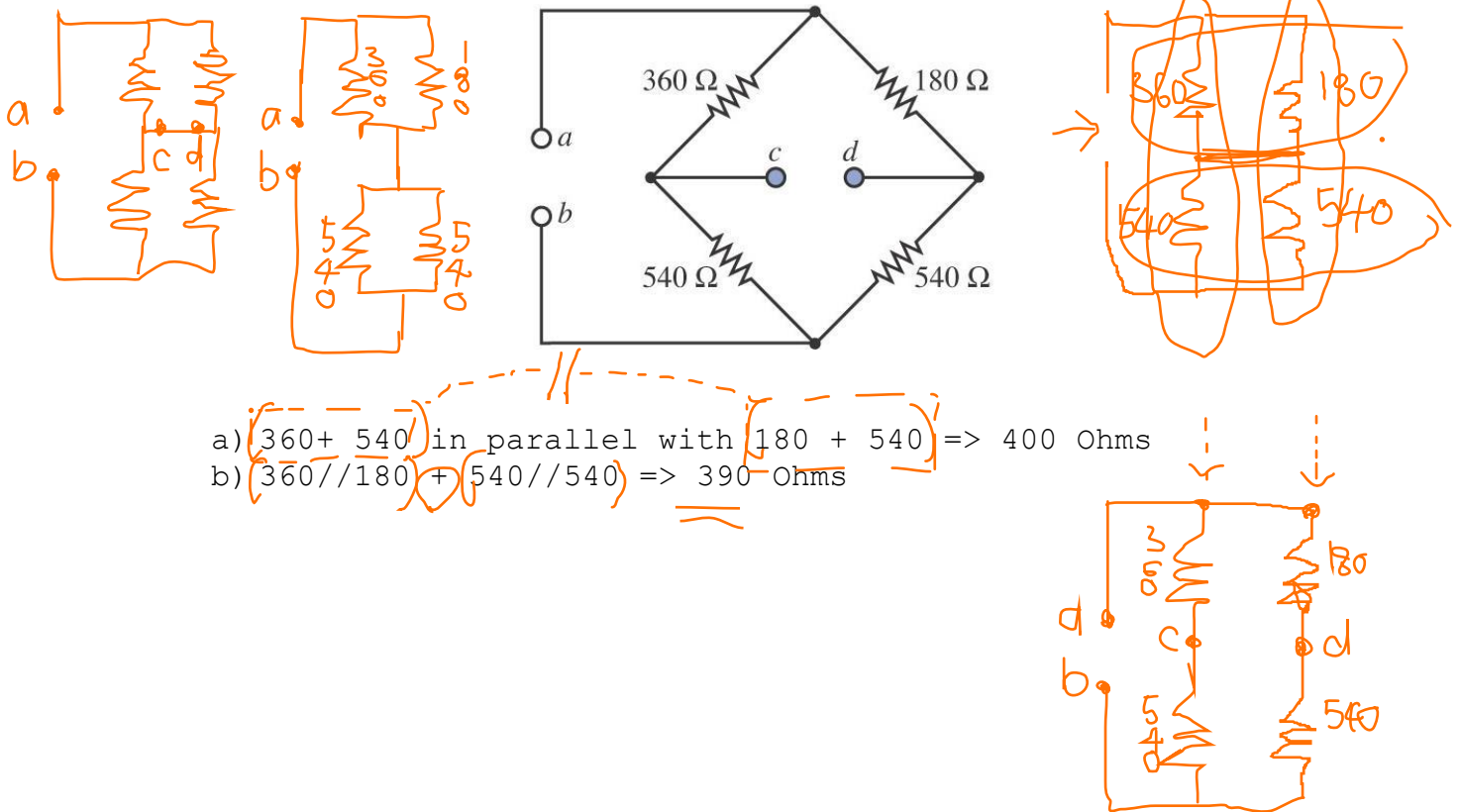


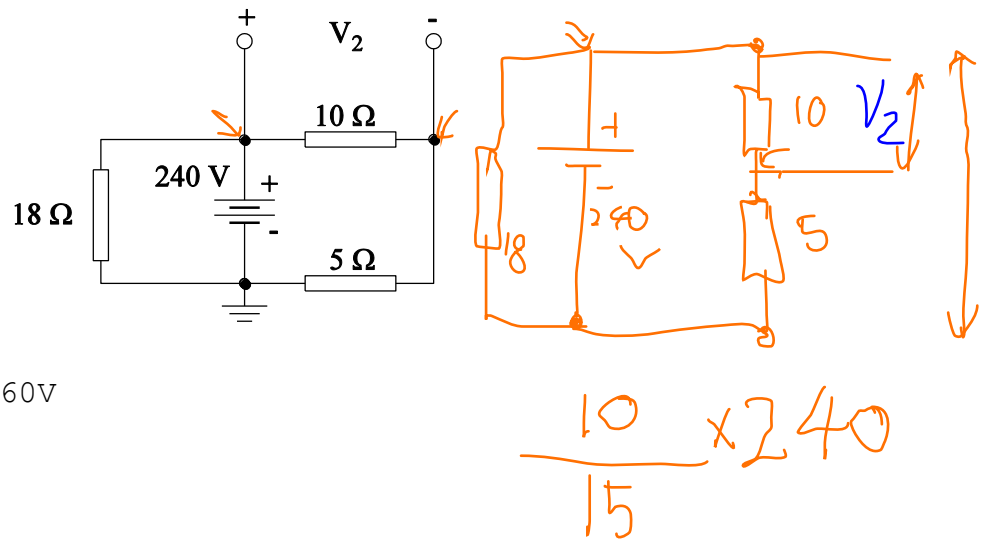QUESTION 2 -

Using the voltage divider rule, determine the voltage V_2 .


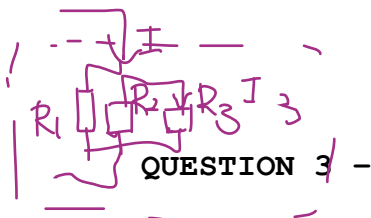
$$V_2 = 240 \times 10 / 15 \Rightarrow 160V$$




$$I_1 = \frac{R_2}{R_1 + R_2} \times I$$


$$V_{24} = I R_{24}$$

- (a) Determine the current in the 24 Ω resistor.
 (b) What is the voltage across the current source?

$$I_3 = \frac{R_T}{R_3} \times I$$

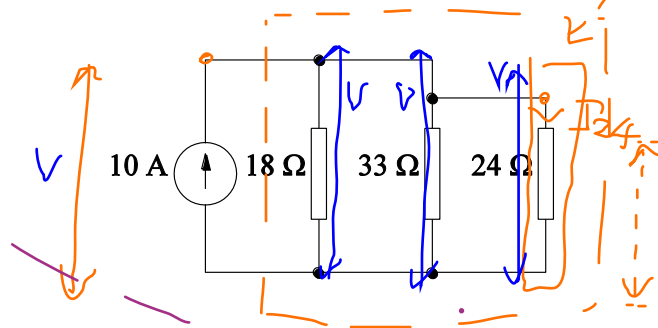
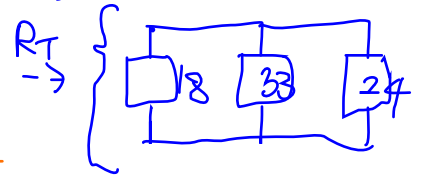
$$\frac{1}{R_T} = \frac{1}{18} + \frac{1}{33} + \frac{1}{24}$$






- (a) Determine Total R first. Then use general form of current divider.

$$R_T = 7.84 \text{ Ohms } I_{24} = 10 \times \frac{7.84}{24} \Rightarrow 3.27 \text{ Amps}$$

- (b) $V = 24 \times 3.27 \Rightarrow 78.42 \text{ V}$

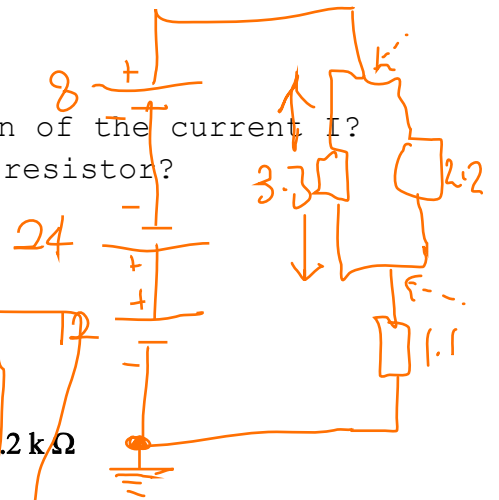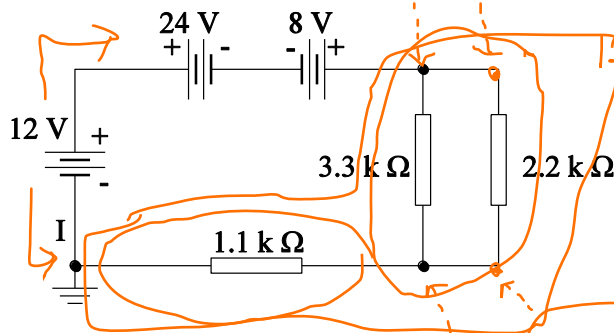
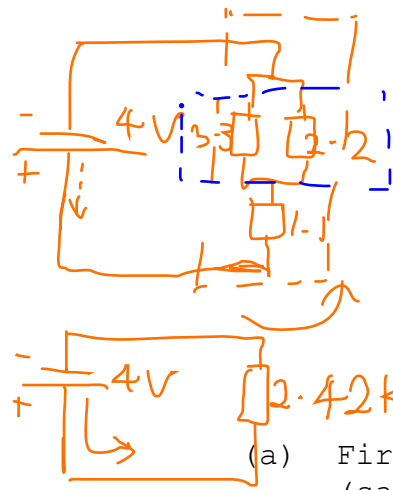
QUESTION 4 -

- What is the magnitude and the direction of the current I ?
- What is the voltage across the $3.3\text{ k}\Omega$ resistor?




- First group all the voltage sources. $\Rightarrow 12 - 24 + 8 \Rightarrow -4\text{V}$ (same polarity as the 24V source). Determine Total R. $R = 1.1\text{K} + [3.3//2.2] \Rightarrow 2.42\text{k}$ Hence current is $4/2.42\text{K} \Rightarrow 1.65\text{ mA}$ flowing anti clock wise in the circuit.
- $V = 4 \times 1.32 / 2.42 \Rightarrow 2.18\text{V}$ (the 1.32K being the total resistance of the 3.3 and 2.2K resistors)

$$I = \frac{4}{2.42}$$

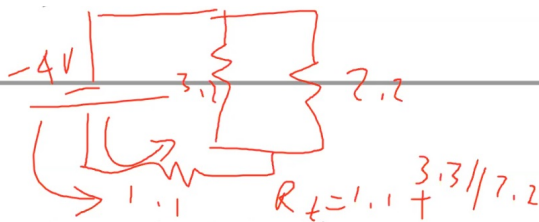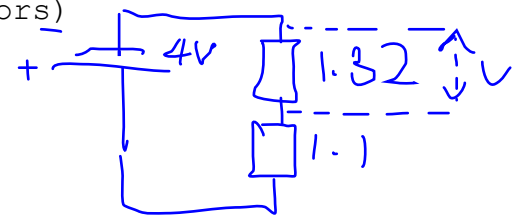


$$R_t = 1.1 + \frac{3.3 \times 2.2}{3.3 + 2.2} = 2.42\text{ k}\Omega$$

$$I = \frac{4}{2.42} = 1.65\text{ mA}$$

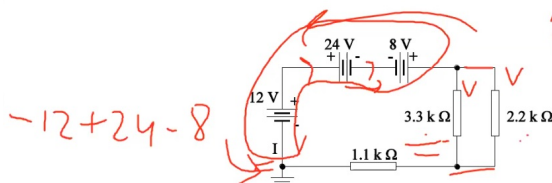

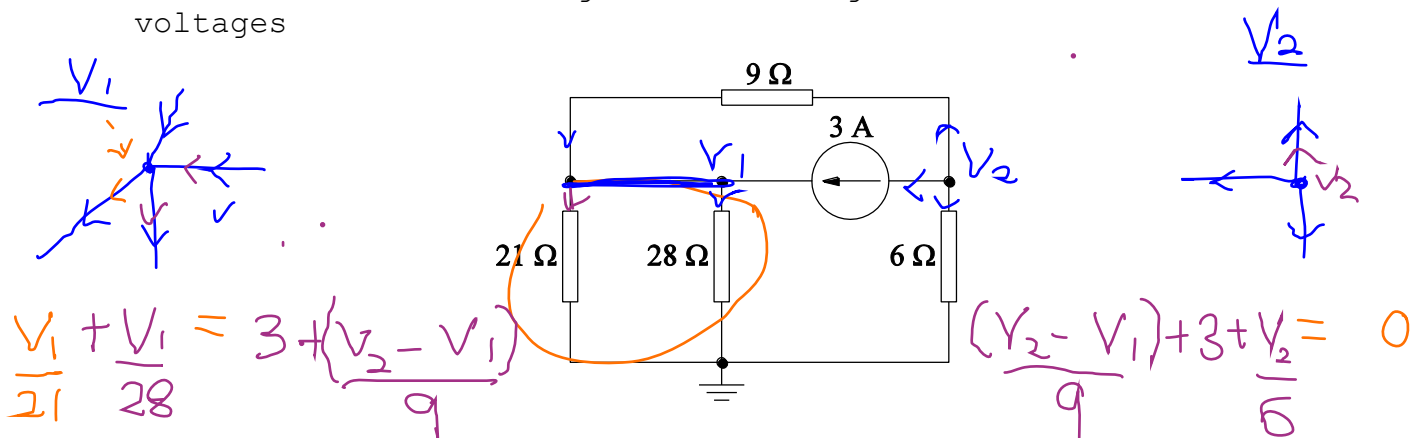QUESTION 5

Using Nodal Analysis techniques, write the equations for the node voltages using the system ground as the reference node. Indicate the node voltages on the diagram. Solve for the nodal voltages



Combine 21 and 28 ohm resistors into one (they share a single node) \Rightarrow 12 Ohm resistor


$$-(1/12 + 1/9)V_1 + (1/9)V_2 = -3$$

$$(1/9)V_1 - (1/6 + 1/9)V_2 = 3$$

Solve for V_1 and V_2

KCL Node ①
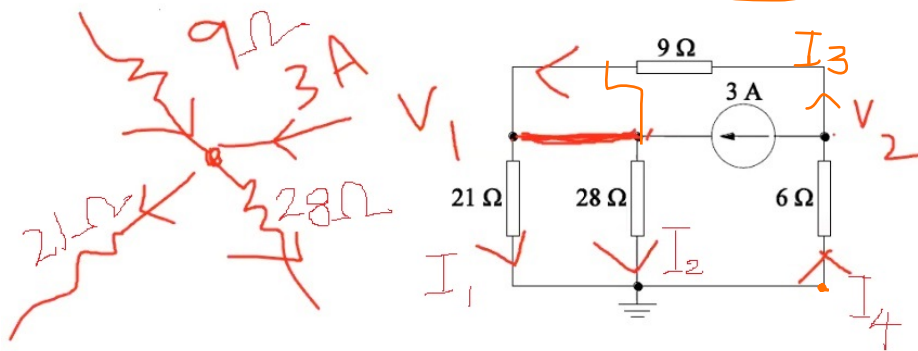
$$3A + \frac{V_2 - V_1}{9} = \frac{V_1 - 0}{21} + \frac{V_1 - 0}{28}$$



KCL V_2

$$I_4 = 3 + I_3$$

$$\frac{0 - V_2}{6} = 3 + \frac{V_2 - V_1}{9}$$

QUESTION 6


Find the

(a) Thévenin equivalent circuits for the network external to the resistor R_L .

How to find R_{Th}

What is the value of R_{Th}

How to find V_{Th}

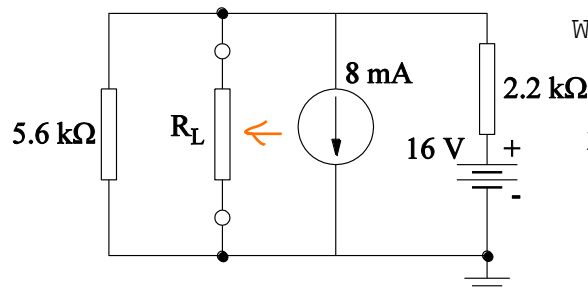

There are 2 sources, either use super position or convert current to voltage source (with 5.6K resistor) and solve


For R_{Th} , open current source and short out voltage source..

$$R_{Th} = 5.6 // 2.2 \Rightarrow 1.58 \text{ K Ohms}$$

Voltage due to 8mA source is -12.64V







Voltage due to 16V source is 11.49 V

$$R_{th} = 5.6 // 2.2$$

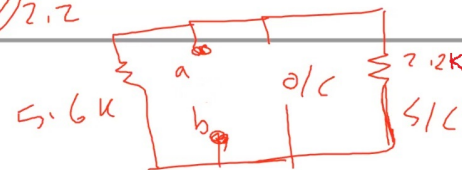


Superposition theorem

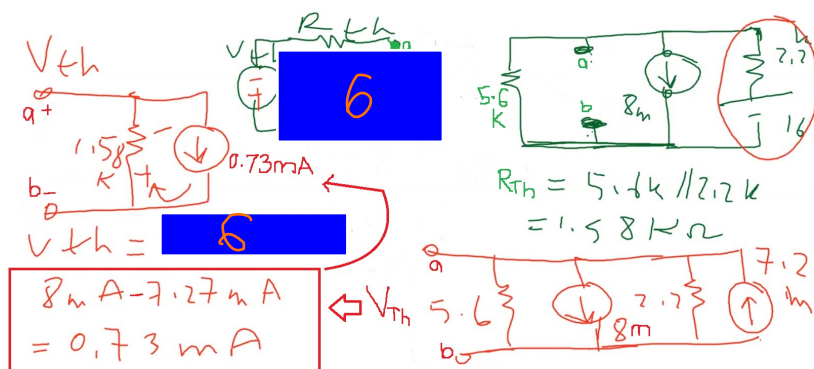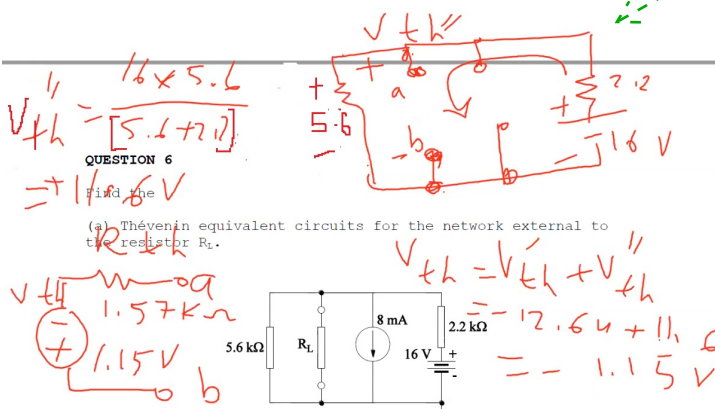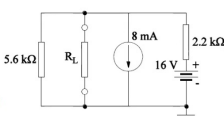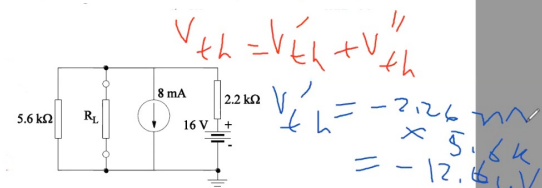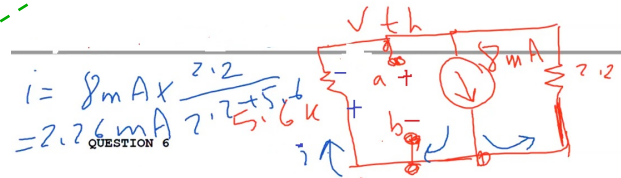
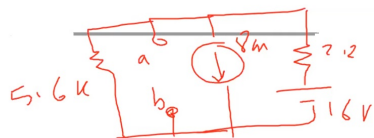
$$E_{th} = -12.64 + 11.49 = -1.15 \text{ V}$$



Source Transformation

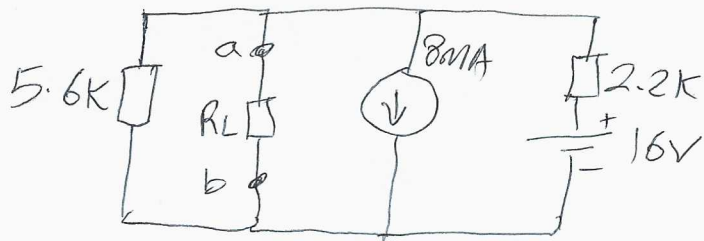


Find R_{TH}

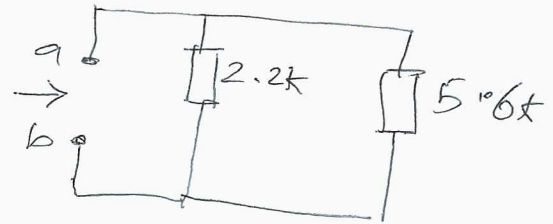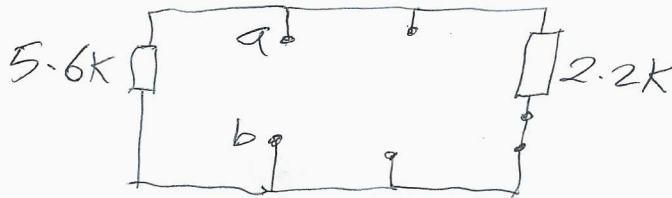


$$R_{TH} = \frac{(2.2k)(5.6k)}{(2.2k) + (5.6k)}$$

$$R_{TH} = 1.58k\Omega$$

Superposition theorem

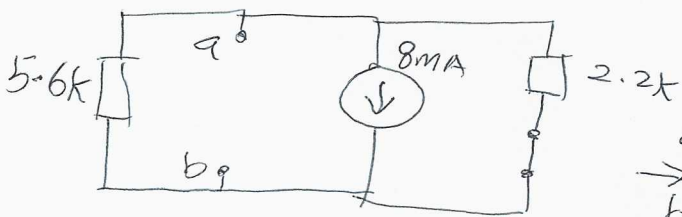


(current divider)

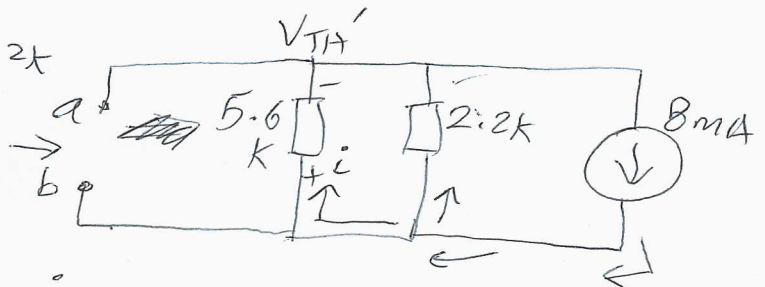


$$\begin{aligned} I_{5.6k} &= 8mA \times \frac{2.2k}{5.6k + 2.2k} \\ &= 2.256mA \end{aligned}$$
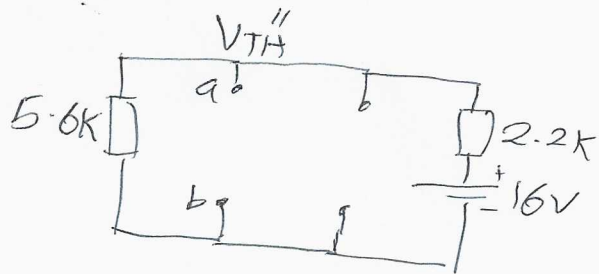
$$\begin{aligned} V_{TH}' &= -I(5.6k) \\ &= -(2.256mA)(5.6k\Omega) \\ &= -12.63V \end{aligned}$$



\Rightarrow

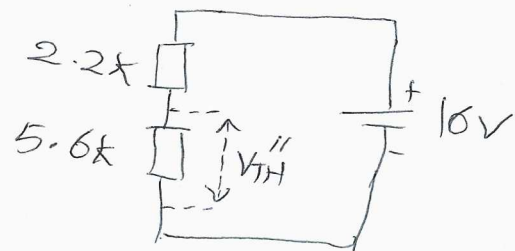

(Voltage divider)


$$V_{TH}'' = \frac{5.6k}{5.6k + 2.2k} \times 16V$$

$$V_{TH}'' = 11.49V$$



$$V_{TH} = V_{TH}' + V_{TH}''$$

$$V_{TH} = -12.63 + 11.49 = -1.14V$$


~~Using source conversion~~

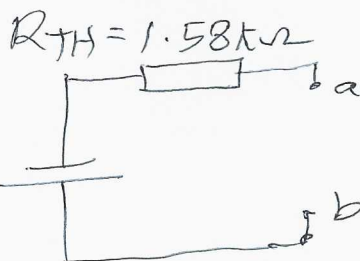


Using source conversion

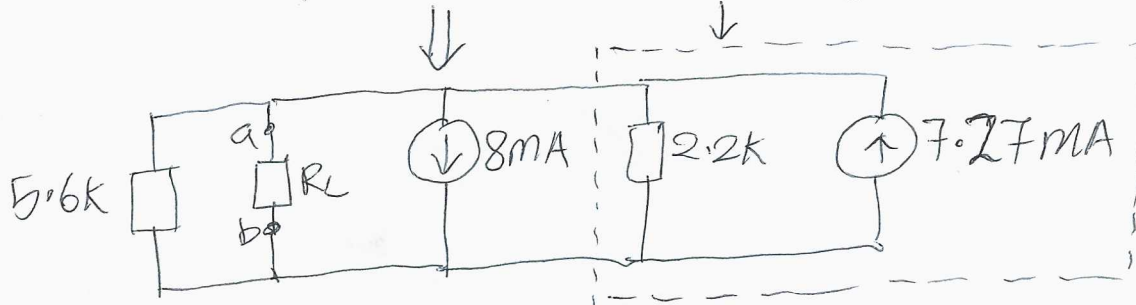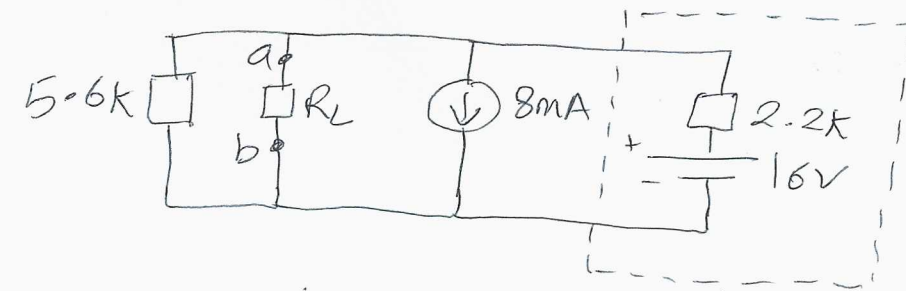
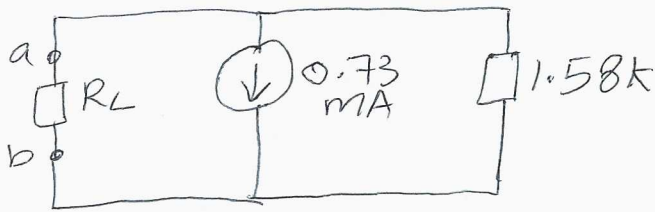
$$R_T = \frac{(5.6k)(2.2k)}{(5.6k) + (2.2k)} = 1.58k\Omega$$




Find R_{TH}

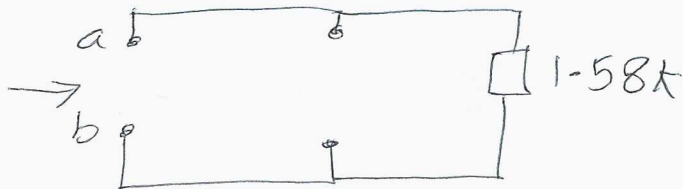

$$R_{TH} = 1.58k\Omega$$

Find V_{TH}

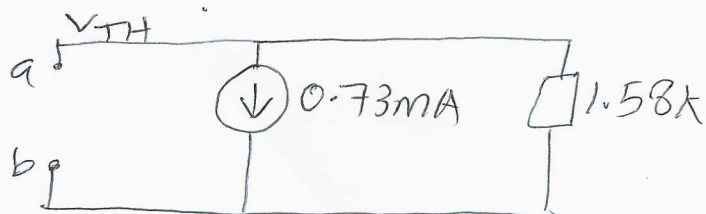

$$\begin{aligned} V_{TH} &= -(0.73mA)(1.58k\Omega) \\ &= -1.15V \end{aligned}$$