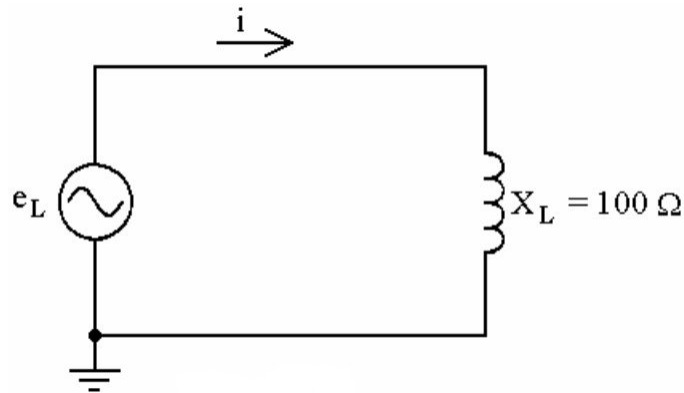


# **ENGG104 Tutorial 9 extra Problems (revision)**

Name\_\_\_\_\_

Student Number\_\_\_\_\_

**MULTIPLE CHOICE. Choose the one alternative that best completes the statement or answers the question.**



**Figure 14.1**

- 1) See Figure 14.1. What is the coil current if  $e_L$  is  $500 \sin(50t + 20^\circ)$ ? 1) \_\_\_\_\_
- A)  $5 \sin 50t$  B)  $5 \sin(50t - 70^\circ)$
- C)  $5 \sin(50t + 20^\circ)$  D)  $5 \sin(50t + 110^\circ)$

**TRUE/FALSE. Write 'T' if the statement is true and 'F' if the statement is false.**

- 2) The length of a phasor is called the modulus or magnitude. 2) \_\_\_\_\_

**MULTIPLE CHOICE. Choose the one alternative that best completes the statement or answers the question.**

- 3) Which one of the following rectangular values is equivalent to the polar form  $20 \angle 55^\circ$ ? 3) \_\_\_\_\_
- A)  $16.4 - j11.5$  B)  $11.5 + j16.4$  C)  $11.5 - j16.4$  D)  $16.4 + j11.5$

**TRUE/FALSE. Write 'T' if the statement is true and 'F' if the statement is false.**

- 4) Unlike inductive reactance, capacitive reactance dissipates energy in the form of heat. 4) \_\_\_\_\_

**MULTIPLE CHOICE. Choose the one alternative that best completes the statement or answers the question.**

- 5) At what frequency does a  $10 \mu\text{F}$  capacitor have a reactance of  $100 \Omega$ ? 5) \_\_\_\_\_
- A) 159 Hz B) 1.59 MHz C) 15.9 kHz D) 1.59 kHz

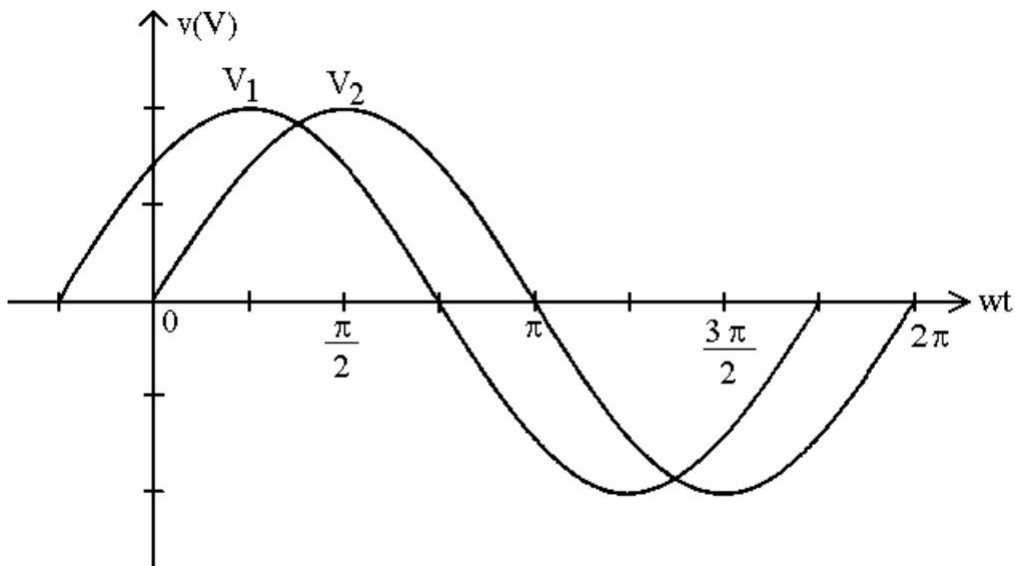


Figure 14.3

- 6) See Figure 14.3. What relationship exists between voltages  $v_1$  and  $v_2$ ? 6) \_\_\_\_\_
- A)  $v_1$  lags  $v_2$  by  $(\pi/4)^\circ$ . B)  $v_1$  leads  $v_2$  by  $45^\circ$ .  
 C)  $v_1$  leads  $v_2$  by  $(\pi/4)^\circ$ . D)  $v_1$  lags  $v_2$  by  $45^\circ$ .

**TRUE/FALSE.** Write 'T' if the statement is true and 'F' if the statement is false.

- 7) The derivative of a sine wave is a cosine wave. 7) \_\_\_\_\_

**SHORT ANSWER.** Write the word or phrase that best completes each statement or answers the question.

- 8) Convert  $4 - j3$  to polar form. 8) \_\_\_\_\_

**MULTIPLE CHOICE.** Choose the one alternative that best completes the statement or answers the question.

- 9) The average power, or real power is the power delivered to and dissipated by the \_\_\_\_\_. 9) \_\_\_\_\_
- A) Inductor B) Capacitor C) Resistor D) Load

**SHORT ANSWER.** Write the word or phrase that best completes each statement or answers the question.

- 10) Reduce the expression  $5 \angle 60^\circ + 3 \angle -20^\circ$ , leaving your answer in rectangular form. 10) \_\_\_\_\_

- 11) Change  $0 - j25$  to polar form. 11) \_\_\_\_\_

**MULTIPLE CHOICE.** Choose the one alternative that best completes the statement or answers the question.

- 12) If the voltage  $v = 50 \sin(500t - 75^\circ)$  is impressed across a  $25 \Omega$  resistor, which equation describes the resistor current? 12) \_\_\_\_\_
- A)  $2 \sin(500t - 75^\circ)$  B)  $1250 \sin(500t - 75^\circ)$   
 C)  $2 \cos(500t - 75^\circ)$  D)  $2 \sin(20t - 3^\circ)$

13) Which relationship is true of *power factor*?

13) \_\_\_\_\_

- A) The power factor is the ratio of the total power in a circuit to the circuit current.
- B) The power factor will be lagging in a capacitive circuit.
- C) The more resistive the total impedance, the closer the power factor is to 1.
- D) The more resistive the total impedance, the closer the power factor is to 0.

**TRUE/FALSE.** Write 'T' if the statement is true and 'F' if the statement is false.

14) For a purely resistive element, the voltage and the current through the element are in phase.

14) \_\_\_\_\_

15) Inductive reactance increases directly in proportion to frequency.

15) \_\_\_\_\_

**SHORT ANSWER.** Write the word or phrase that best completes each statement or answers the question.

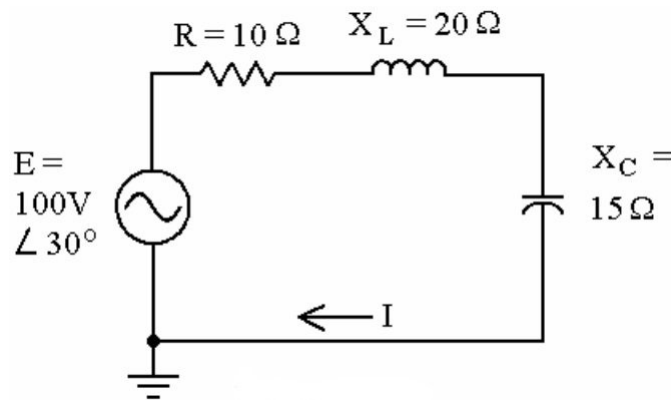


Figure 15.3

16) See Figure 15.3. Use the voltage divider rule to calculate the voltage across the coil.

16) \_\_\_\_\_

**TRUE/FALSE.** Write 'T' if the statement is true and 'F' if the statement is false.

17) For parallel elements, the element with the smallest impedance will have the least impact on the total impedance at that frequency.

17) \_\_\_\_\_

**MULTIPLE CHOICE.** Choose the one alternative that best completes the statement or answers the question.

18) Express the impedance of a 10  $\mu\text{F}$  capacitor at 60 Hz in rectangular form.

18) \_\_\_\_\_

- A)  $0 \Omega - j265.3 \Omega$
- B)  $0 \Omega - j0.00377 \Omega$
- C)  $265.3 \Omega - j0 \Omega$
- D)  $0 \Omega + j265.3 \Omega$

**TRUE/FALSE.** Write 'T' if the statement is true and 'F' if the statement is false.

19) The basic format for the voltage divider rule in ac circuits is unlike that for dc circuits.

19) \_\_\_\_\_

**SHORT ANSWER.** Write the word or phrase that best completes each statement or answers the question.

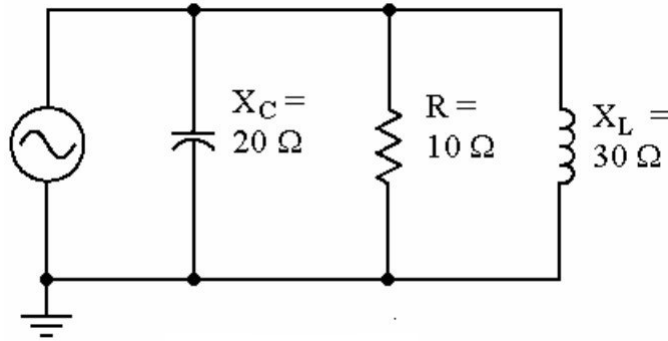


Figure 15.5

20) See Figure 15.5. Sketch the impedance diagram for this circuit.

20) \_\_\_\_\_

**MULTIPLE CHOICE.** Choose the one alternative that best completes the statement or answers the question.

21) What is the reactance of a 25 millihenry coil at 600 hertz?

A) 785 ohms

B) 94,000 ohms

C) 94 ohms

D) 0.011 ohms

21) \_\_\_\_\_

22) Ignoring capacitive effects, what is the impedance of a 250 mH coil with an internal resistance of 55 ohms at 60 Hz?

A) 94.2 ohms

B) 149.2 ohms

C) 109 ohms

D) 10,900 ohms

22) \_\_\_\_\_

**TRUE/FALSE.** Write 'T' if the statement is true and 'F' if the statement is false.

23) Inductive reactance is plotted on the negative imaginary axis on an impedance diagram.

23) \_\_\_\_\_

**MULTIPLE CHOICE.** Choose the one alternative that best completes the statement or answers the question.

24) A measure of how well an ac circuit will admit, or allow current to flow in the circuit is \_\_\_\_\_.

A) Resistance

B) Inductance

C) Admittance

D) Capacitance

24) \_\_\_\_\_

25) Ignoring any effects of dc resistance, what is the total reactance of a 250 mH coil in series with a 4.7 microfarad capacitor at a signal frequency of 60 Hz?

A) 659 ohms

B) 111 ohms

C) 113 ohms

D) 470 ohms

25) \_\_\_\_\_

**TRUE/FALSE.** Write 'T' if the statement is true and 'F' if the statement is false.

26) Power factor can be determined by forming the ratio of the total circuit resistance to the magnitude of the total circuit impedance.

26) \_\_\_\_\_

**MULTIPLE CHOICE.** Choose the one alternative that best completes the statement or answers the question.

27) Which one of the following is true of ac circuits with reactive elements?

A) Depending on the frequency applied, the circuit can look either inductive or capacitive.

B) The magnitude of the voltage across any one element can never exceed the applied voltage.

C) The smaller the resistive element of a circuit, the closer the power factor is to unity.

D) The impedance of any one element can never exceed the total network impedance.

27) \_\_\_\_\_


**TRUE/FALSE. Write 'T' if the statement is true and 'F' if the statement is false.**

28) The advantage of an impedance diagram is that it will reflect all impedance on the positive real axis. 28) \_\_\_\_\_

29) Impedance is the combination of capacitive reactance, inductive reactance, and dc resistance. 29) \_\_\_\_\_

**MULTIPLE CHOICE. Choose the one alternative that best completes the statement or answers the question.**

30) Ignoring inductive effects, what is the impedance of a RC series capacitor made up of a 56 Kilohm resistor and a 0.033 microfarad capacitor at a signal frequency of 450 Hz? 30) \_\_\_\_\_  
 A) 10.7 kilohms B) 66.7 kilohms C) 45.3 kilohms D) 57.0 kilohms

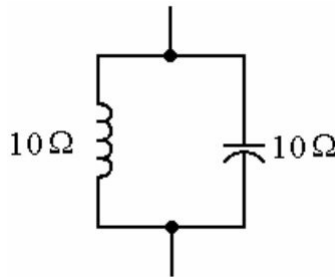


**Figure 16.2**

31) See Figure 16.2. What is the total impedance  $Z_T$  for this circuit? 31) \_\_\_\_\_  
 A)  $100\ \Omega \angle 0^\circ$  B)  $0\ \Omega \angle 0^\circ$  C)  $5\ \Omega \angle 0^\circ$  D) infinity

**TRUE/FALSE. Write 'T' if the statement is true and 'F' if the statement is false.**

32) The equivalent circuit is used in determining the source current in series-parallel ac networks. 32) \_\_\_\_\_

**MULTIPLE CHOICE. Choose the one alternative that best completes the statement or answers the question.**

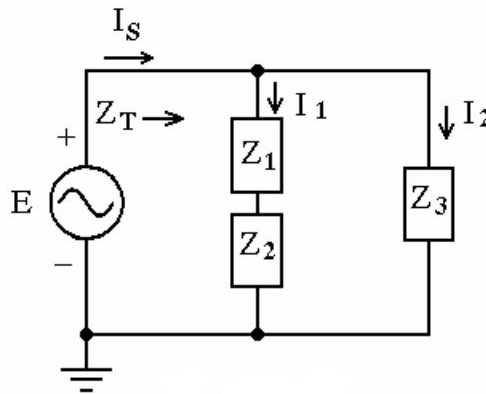

**Figure 16.3**

33) See Figure 16.3. Which one equation describes source voltage E? 33) \_\_\_\_\_  
 A)  $E = I_S^2 Z_T$  B)  $E = I_S \div Z_T$  C)  $E = I_S Z_T$  D)  $E = Z_T \div I_S$

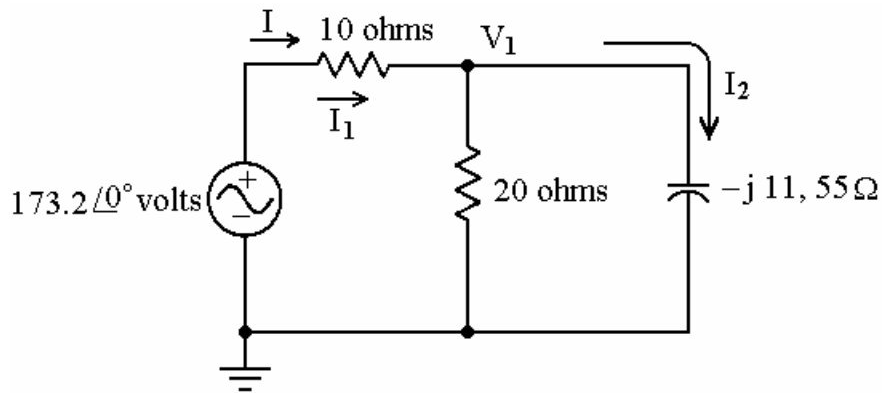


Figure 16.9

- 34) For the circuit shown in Figure 16.9, the current flowing through the 10 Ω resistor is 34) \_\_\_\_\_  
 A)  $5 \angle -30^\circ$  B)  $10 \angle 30^\circ$  C)  $173.2 \angle 0^\circ$  D)  $8.66 \angle 60^\circ$

**TRUE/FALSE. Write 'T' if the statement is true and 'F' if the statement is false.**

- 35) The use of a ground fault circuit interrupter does not mean a person will not receive a shock, however it will shut off power quickly. 35) \_\_\_\_\_

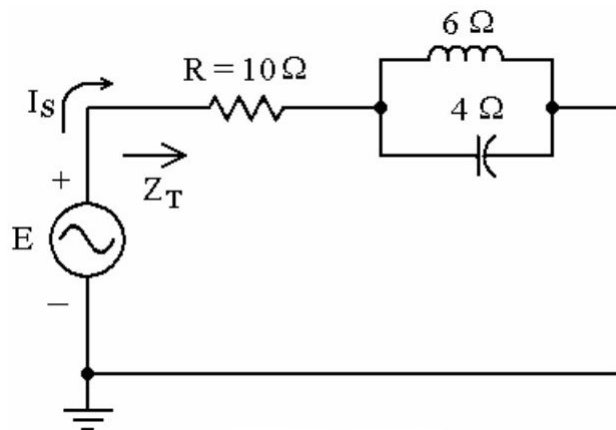


Figure 16.1

- 36) See Figure 16.1.  $I_S$  may be found by dividing  $E$  by  $Z_T$ . 36) \_\_\_\_\_

**SHORT ANSWER. Write the word or phrase that best completes each statement or answers the question.**

- 37) For many single source, series-parallel networks, the analysis is one that works back to the source, determines the \_\_\_\_\_, and then finds its way to the desired unknown. 37) \_\_\_\_\_

**MULTIPLE CHOICE.** Choose the one alternative that best completes the statement or answers the question.

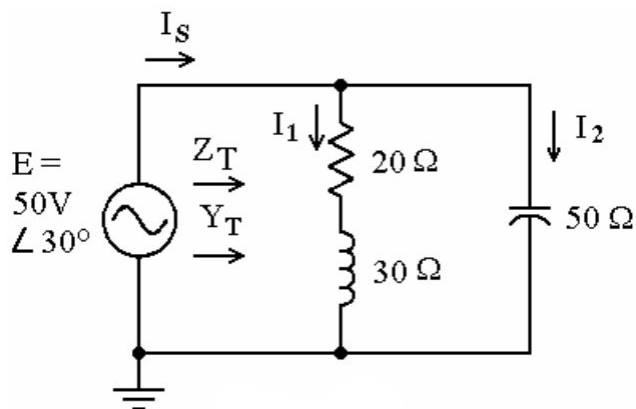


Figure 16.5

38) See Figure 16.5. What is the value of current  $I_2$ ?

A)  $1.39 \text{ A } \angle -26.3^\circ$

B)  $1 \text{ A } \angle 120^\circ$

C)  $0.72 \text{ A } \angle 26.3^\circ$

D)  $1 \text{ A } \angle -120^\circ$

38) \_\_\_\_\_

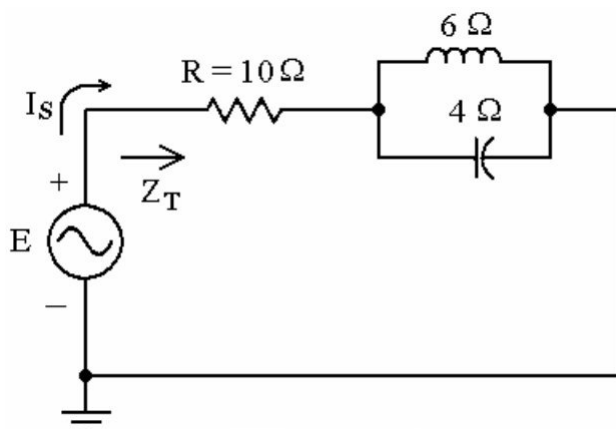


Figure 16.1

39) See Figure 16.1. What is the total impedance  $Z_T$  of this circuit?

A)  $10 \Omega + j12 \Omega$

B)  $10 \Omega - j12 \Omega$

C)  $10 \Omega - j2 \Omega$

D)  $10 \Omega - j2.4 \Omega$

39) \_\_\_\_\_

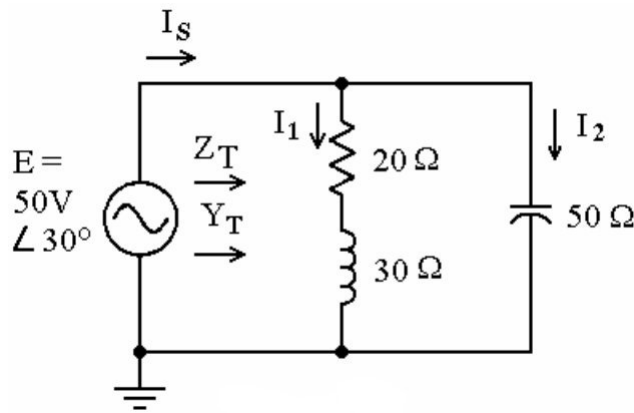


Figure 16.5

- 40) See Figure 16.5. What is the value of current  $I_1$ ? 40) \_\_\_\_\_  
 A) 1 A  $\angle -120^\circ$  B) 1 A  $\angle 120^\circ$  C) 0.72 A  $\angle 26.3^\circ$  D) 1.39 A  $\angle -26.3^\circ$

**TRUE/FALSE.** Write 'T' if the statement is true and 'F' if the statement is false.

- 41) The higher the frequency, the better the short-circuit approximation for  $X_C$  for ac conditions. 41) \_\_\_\_\_  
 42) Determining the source current is the most critical step in solving series-parallel ac networks. 42) \_\_\_\_\_  
 43) In a series-parallel circuit, if  $e = 50 \text{ V } \angle 20^\circ$  and  $i = 25 \text{ A } \angle 20^\circ$ , then the total impedance  $Z_T$  is purely resistive. 43) \_\_\_\_\_

**SHORT ANSWER.** Write the word or phrase that best completes each statement or answers the question.


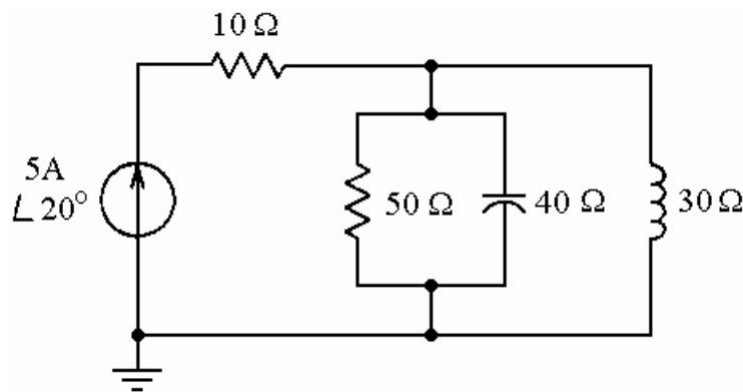


Figure 16.7

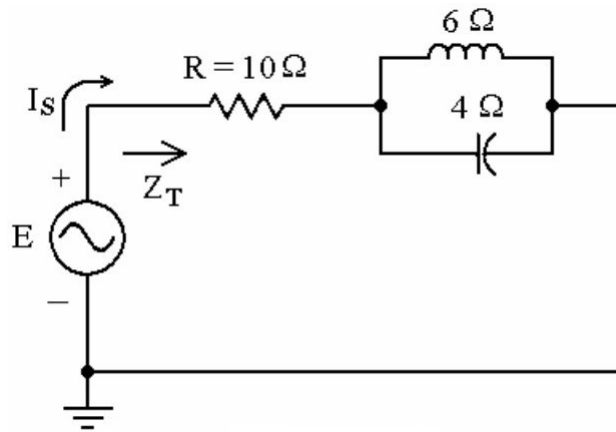- 44) See Figure 16.7. Find the voltage across the coil. 44) \_\_\_\_\_



**MULTIPLE CHOICE.** Choose the one alternative that best completes the statement or answers the question.



**Figure 16.1**

- 45) A 1 kHz signal  $E$  is applied in the circuit shown in Figure 16.1. What is the value of inductor  $L$ ?
- A) 1910  $\mu\text{H}$       B) 955  $\mu\text{H}$       C) 1047  $\mu\text{H}$       D) 26.5  $\mu\text{H}$

45) \_\_\_\_\_